



# **COL215 DIGITAL LOGIC AND SYSTEM DESIGN**

Introduction to VHDL

11 August 2017

# Why HDLs (Hardware Description Language)

- Schematic diagrams are tedious and error prone for large circuits
- Schematic diagrams provide only structural abstraction, HDLs provide structural as well as behavioural abstraction
- Behavioural abstraction increases the scope of design automation

# VHDL: Basic units

- Basic unit of description is an ENTITY - ARCHITECTURE pair
- ENTITY defines the exterior
- ARCHITECTURE defines the interior
  - structural
  - behavioral
- Multiple architectures possible for same entity

# VHDL: information carriers


## Physical

- PORTS - external
- SIGNALS - internal
  - Can be simply wires or have registers

## Abstract


- Variables
  - may or may not correspond to physical objects

# Interfaces: entities and ports

 

```
ENTITY and_gate IS  
  PORT (a: IN BIT;  
        b: IN BIT;  
        y: OUT BIT);  
END and_gate;
```

# Functionality: architectures

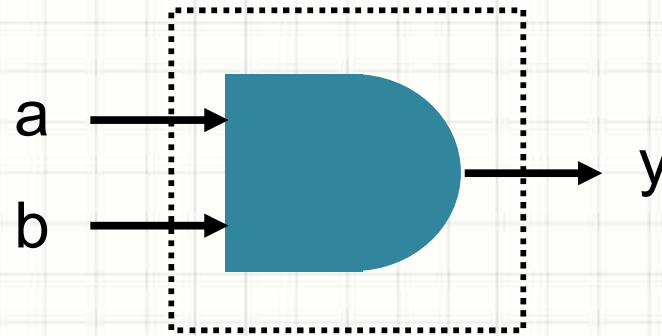

```
ARCHITECTURE data_flow OF and_gate IS  
BEGIN  
    y <= a AND b;  
END data_flow;
```

# Meaning of signal assignment

$y \leq a \text{ AND } b;$

Assignment: compute RHS, assign  
computed value to LHS

When is it executed? Notion of time?

Once initially, then every time there is a  
change in the value of a or b.

It is considered to be **sensitive** to a and b.



# Combinational circuit example

```
ENTITY cc IS  
  PORT (a, b, c, d: IN BIT;  
        y: OUT BIT);  
END cc;
```

```
ARCHITECTURE dd OF cc IS  
  BEGIN
```

```
    y <= a AND (b OR c) OR NOT a AND (c OR d);
```

```
  END dd;
```

Signal Assignment




Does this expression  
imply a structure?



 
# Implementation - 1

$y \leq a \text{ AND } (b \text{ OR } c) \text{ OR NOT } a \text{ AND } (c \text{ OR } d);$


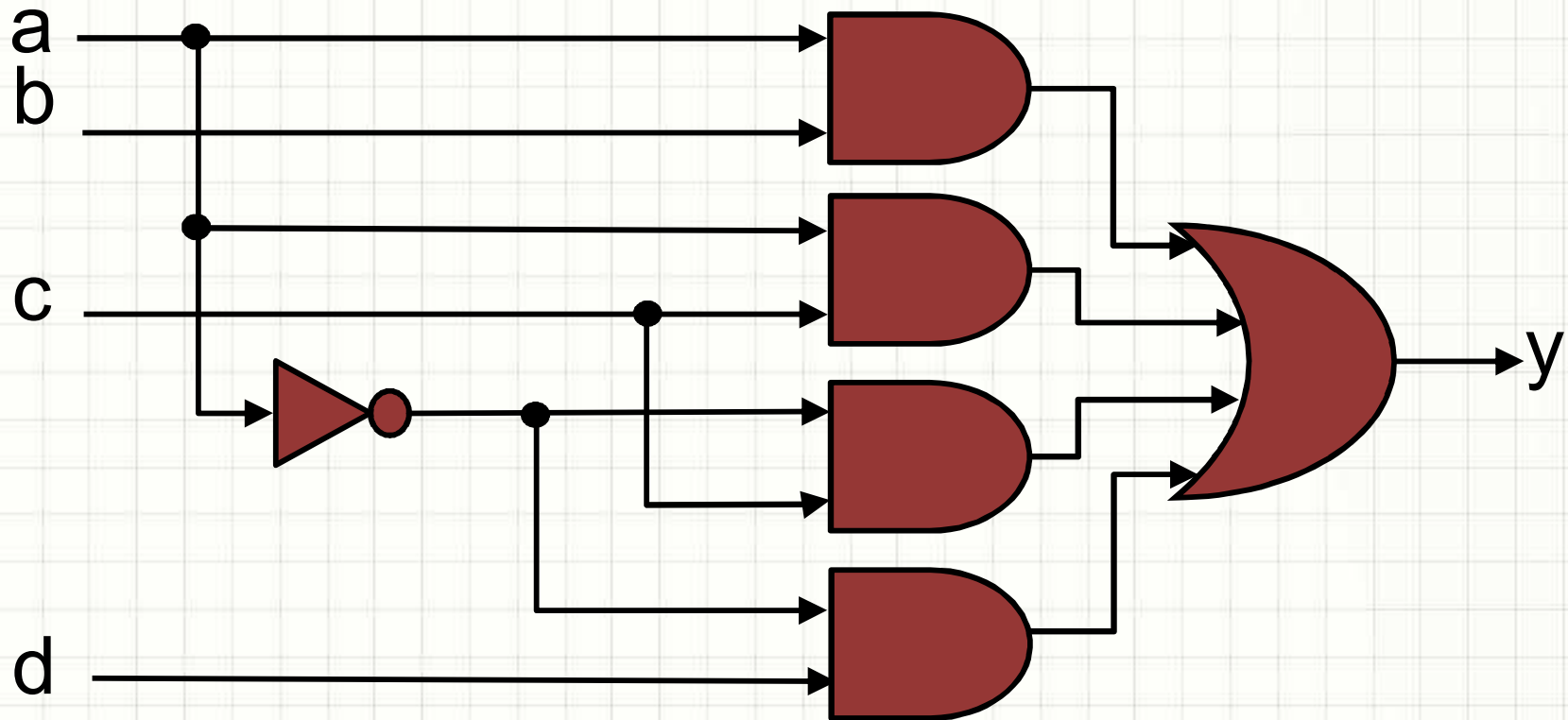
# Implementation - 2

$y \leq a \text{ AND } (b \text{ OR } c) \text{ OR NOT } a \text{ AND } (c \text{ OR } d);$



# Combinational circuit example

ENTITY cc IS PORT (a, b, c, d: IN BIT; y: OUT BIT); END cc;



ARCHITECTURE dd OF cc IS  
BEGIN

`y <= a AND (b OR c) OR NOT a AND (c OR d);`

END dd;

Signal Assignment



Which structure is implied ?

  

# Circuit with multiple outputs

```
ARCHITECTURE data_flow  
OF full_adder IS  
BEGIN  
    si <= ai XOR bi XOR ci;  
    co <= (ai AND bi) OR (bi AND ci)  
        OR (ai AND ci);  
END data_flow;
```

Concurrent Signal Assignments

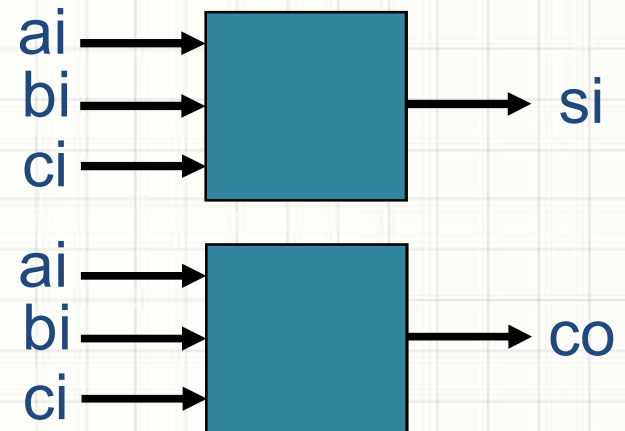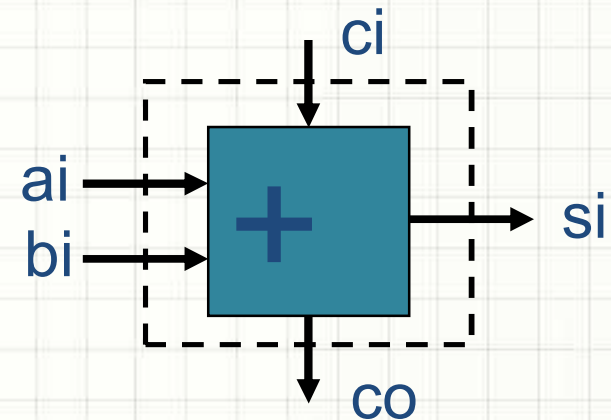

# Is the order significant?



```
ARCHITECTURE data_flow1 OF full_adder IS  
BEGIN
```

```
    si <= ai XOR bi XOR ci;
```

```
    co <= (ai AND bi) OR (bi AND ci) OR (ai AND ci);
```

```
END data_flow1;
```

```
ARCHITECTURE data_flow2 OF full_adder IS  
BEGIN
```

```
    co <= (ai AND bi) OR (bi AND ci) OR (ai AND ci);
```

```
    si <= ai XOR bi XOR ci;
```

```
END data_flow2;
```



**THANKS**