 


NAME:

ENTRY No.:

1. Write a Boolean expression to represent the function implemented by the circuit shown. There is no need to draw truth table or Karnaugh map.



[2]

Solution:

Denoting the multiplexer inputs as x_0 , x_1 , x_2 and x_3 , we can express f as follows.

$$f = \text{enable} \cdot (s_1' \cdot s_0' \cdot x_0 + s_1' \cdot s_0 \cdot x_1 + s_1 \cdot s_0' \cdot x_2 + s_1 \cdot s_0 \cdot x_3),$$

where s_1 and s_0 are the two bits of input s .

We can replace x_0 , x_1 , x_2 , x_3 and enable by '0', $(a \cdot b)'$, $(a + b)'$, '1' and '1' respectively. This leads to the following expression for f .

$$\begin{aligned} f &= 1 \cdot (s_1' \cdot s_0' \cdot 0 + s_1' \cdot s_0 \cdot (a \cdot b)' + s_1 \cdot s_0' \cdot (a + b)' + s_1 \cdot s_0 \cdot 1) \\ &= s_1' \cdot s_0 \cdot (a \cdot b)' + s_1 \cdot s_0' \cdot (a + b)' + s_1 \cdot s_0 \\ &= s_1' \cdot s_0 \cdot a' + s_1' \cdot s_0 \cdot b' + s_1 \cdot s_0' \cdot a' \cdot b' + s_1 \cdot s_0 \end{aligned}$$

This may be simplified to (not required by the question) the following.

$$f = s_0 \cdot a' + s_0 \cdot b' + s_1 \cdot a' \cdot b' + s_1 \cdot s_0$$

NAME:


ENTRY No.:

2. Construct state diagram and state table of a synchronous sequential circuit that looks at input w in frames or sequences of 2 bits. In each frame, it checks if both the bits are identical (both 1's or both 0's). The result of this check is shown on output z during the next frame in both its clock cycles. Output z is made 1 if the bits in the previous frame were identical and made 0 otherwise. Assume that in the initial state, the circuit is ready to start looking at a new frame (i.e., the first 2 bits form the 1st frame, the next 2 bits form the 2nd frame and so on) and z is to be kept 0 during the first frame. The input is synchronized with the clock.

[2]

Solution:

State transition diagram.

 


State table

| Present state | Next state for $w = 0$ | Next state for $w = 1$ | Output z |
|---------------|------------------------|------------------------|------------|
| S0 | S1 | S2 | 0 |
| S1 | S3 | S0 | 0 |
| S2 | S0 | S3 | 0 |
| S3 | S4 | S5 | 1 |
| S4 | S3 | S0 | 1 |
| S5 | S0 | S3 | 1 |

NAME:

ENTRY No.:

 3. Behaviour of a circuit with one input w and two outputs Q_1 , Q_2 is depicted by the waveforms shown below. The circuit consists of two JK flip-flops and a combinational circuit that drives their JK inputs. Inputs to this combinational circuit are w and flip-flop outputs. Derive expressions for the functions implemented by this combinational circuit.



[4]

Solution:

Transitions required at various clock edges and corresponding J K values.

| clock edge | w | present Q1 Q2 | next Q1 Q2 | Q1 transition | Q2 transition | J1 K1 | J2 K2 |
|------------|---|---------------|------------|-------------------|-------------------|-------|-------|
| 1 | 0 | 0 0 | 0 0 | $0 \Rightarrow 0$ | $0 \Rightarrow 0$ | 0 - | 0 - |
| 2 | 1 | 0 0 | 1 0 | $0 \Rightarrow 1$ | $0 \Rightarrow 0$ | 1 - | 0 - |
| 3 | 1 | 1 0 | 1 0 | $1 \Rightarrow 1$ | $0 \Rightarrow 0$ | - 0 | 0 - |
| 4 | 0 | 1 0 | 1 1 | $1 \Rightarrow 1$ | $0 \Rightarrow 1$ | - 0 | 1 - |
| 5 | 0 | 1 1 | 1 1 | $1 \Rightarrow 1$ | $1 \Rightarrow 1$ | - 0 | - 0 |
| 6 | 1 | 1 1 | 0 1 | $1 \Rightarrow 0$ | $1 \Rightarrow 1$ | - 1 | - 0 |
| 7 | 1 | 0 1 | 0 1 | $0 \Rightarrow 0$ | $1 \Rightarrow 1$ | 0 - | - 0 |
| 8 | 0 | 0 1 | 0 0 | $0 \Rightarrow 0$ | $1 \Rightarrow 0$ | 0 - | - 1 |
| 9 | 0 | 0 0 | 0 0 | $0 \Rightarrow 0$ | $0 \Rightarrow 0$ | 0 - | 0 - |
| 10 | 1 | 0 0 | 1 0 | $0 \Rightarrow 1$ | $0 \Rightarrow 0$ | 1 - | 0 - |
| 11 | 1 | 1 0 | 1 0 | $1 \Rightarrow 1$ | $0 \Rightarrow 0$ | - 0 | 0 - |
| 12 | 0 | 1 0 | 1 1 | $1 \Rightarrow 1$ | $0 \Rightarrow 1$ | - 0 | 1 - |
| 13 | 0 | 1 1 | 1 1 | $1 \Rightarrow 1$ | $1 \Rightarrow 1$ | - 0 | - 0 |
| 14 | 1 | 1 1 | 0 1 | $1 \Rightarrow 0$ | $1 \Rightarrow 1$ | - 1 | - 0 |
| 15 | 1 | 0 1 | 0 1 | $0 \Rightarrow 0$ | $1 \Rightarrow 1$ | 0 - | - 0 |

Table for J1 K1

| | $Q1' Q2'$ | $Q1' Q2$ | $Q1 Q2$ | $Q1 Q2'$ |
|------|-----------|----------|---------|----------|
| w' | 0 - | 0 - | - 0 | - 0 |
| w | 1 - | 0 - | - 1 | - 0 |

$$J1 = w Q2'$$

$$K1 = w Q2$$

Table for J2 K2

| | $Q1' Q2'$ | $Q1' Q2$ | $Q1 Q2$ | $Q1 Q2'$ |
|------|-----------|----------|---------|----------|
| w' | 0 - | - 1 | - 0 | 1 - |
| w | 0 - | - 0 | - 0 | 0 - |

$$J2 = w' Q1$$

$$K2 = w' Q1'$$

| | |
|-------|------------|
| NAME: | ENTRY No.: |
|-------|------------|

4. Give entity and architecture description in VHDL for a 4 to 2 encoder, a purely combinational circuit. It has two output ports. If exactly one of the 4 inputs is 1, it outputs a 2 bit code on the first port. Otherwise, it indicates an error on the second port. The 2 bit code on the first port indicates which input is 1. In case of error, the code is ignored.

[2]

Solution:

```

ENTITY encoder_4_2 IS
    PORT (X: IN bit_vector (3 DOWNTO 0);
          code: OUT bit_vector (1 DOWNTO 0);
          error: OUT bit
    );
END encoder_4_2;

ARCHITECTURE casestmt OF encoder_4_2 IS
BEGIN
    PROCESS (X)
    BEGIN
        CASE X IS
            WHEN "1000"    => code <= "11"; error <= '0';
            WHEN "0100"    => code <= "10"; error <= '0';
            WHEN "0010"    => code <= "01"; error <= '0';
            WHEN "0001"    => code <= "00"; error <= '0';
            WHEN OTHERS    => code <= "00"; error <= '1';
        END CASE;
    END PROCESS;
END ARCHITECTURE casestmt;

```

alternatively,

```

ARCHITECTURE ssa OF encoder_4_2 IS
BEGIN
    error <= '0' WHEN (X = "1000" or X = "0100" or X = "0010" or X = "0001") ELSE
        '1';
    WITH X SELECT
        code <= "11" WHEN "1000",
            "10" WHEN "0100",
            "01" WHEN "0010",
            "00" WHEN OTHERS;
END ARCHITECTURE ssa;

```