



# **COL215 DIGITAL LOGIC AND SYSTEM DESIGN**

VHDL – Combinational Logic  
Modules


18 August 2017



# Outline


- Combinational logic modules in VHDL
- 3-port switch example

# Combinational Modules

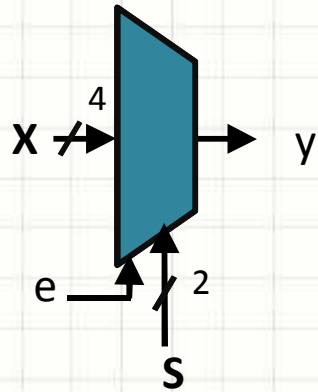


4:1 mux

e	$s_1s_0$	y
0	- -	0
1	00	$x_0$
1	01	$x_1$
1	10	$x_2$
1	11	$x_3$

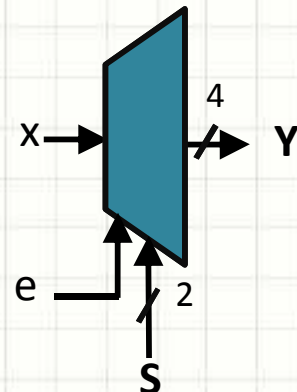


1:4 de-mux

e	$s_1s_0$	$Y_3Y_2Y_1Y_0$
0	- -	0000
1	00	000x
1	01	00x0
1	10	0x00
1	11	x000

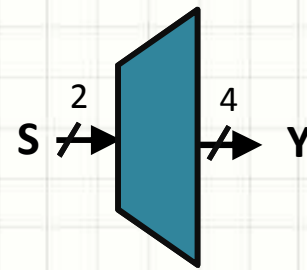

2:4 decoder


$s_1s_0$	$Y_3Y_2Y_1Y_0$
00	0001
01	0010
10	0100
11	1000

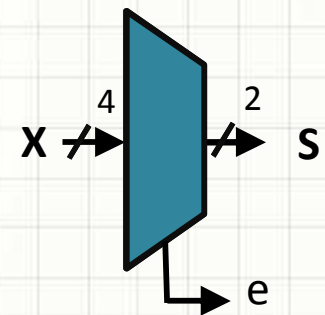


4 input priority encoder

$x_3x_2x_1x_0$	e $s_1s_0$
0000	0 - -
0001	1 00
001-	1 01
01--	1 10
1---	1 11

## Lab exercise 2 : 3-Port Switch

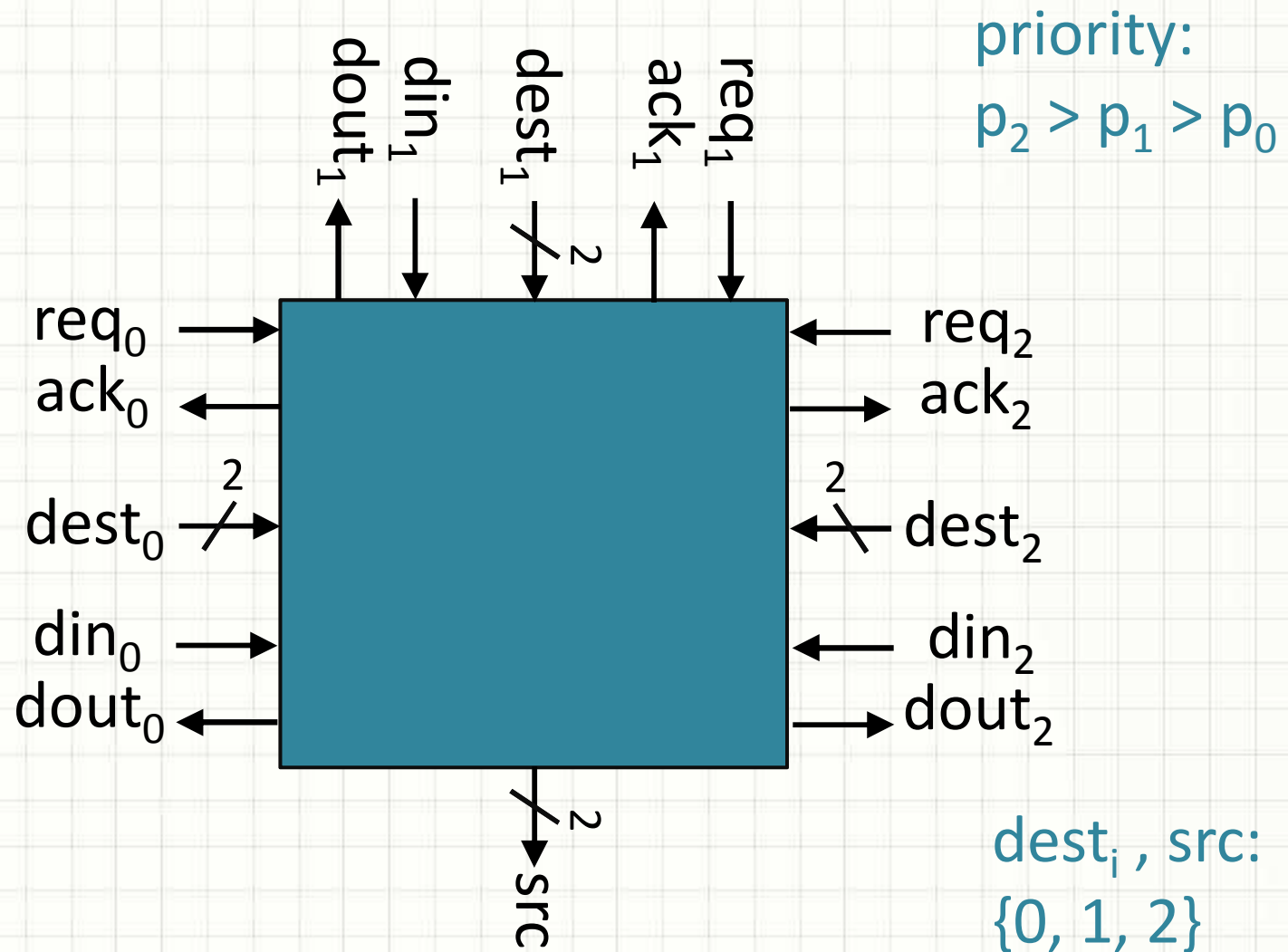


# 3-Port Switch Design

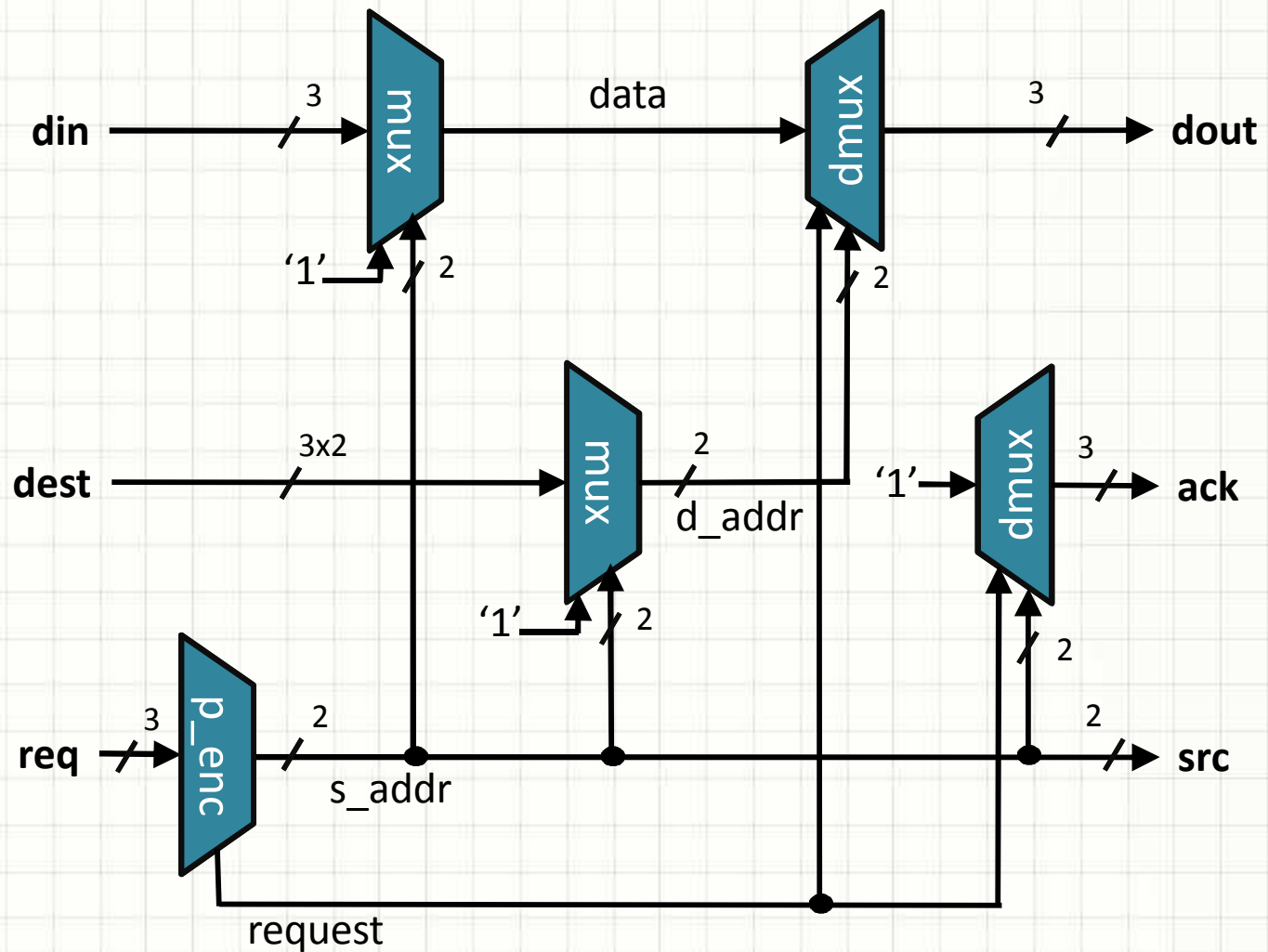

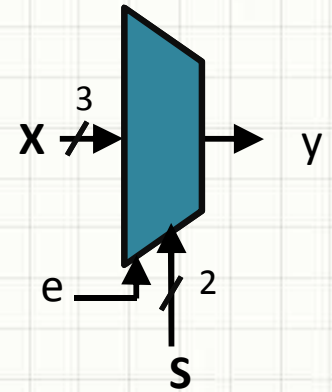
# 3 : 1 Mux

```
ENTITY mux_3_1 IS
  PORT (X: IN    bit_vector (2 DOWNT0 0);
        S: IN    bit_vector (1 DOWNT0 0);
        e: IN    bit;
        y: OUT bit
  );
END mux_3_1;
```


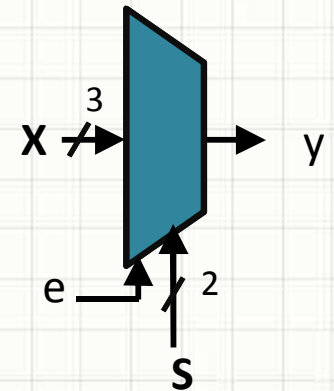
# CASE statement

```
ARCHITECTURE casestmt OF mux_3_1 IS
BEGIN
  PROCESS (S, X, e)
  BEGIN
    IF e = '1' THEN
      CASE S IS
        WHEN "00"      => y <= X(0);
        WHEN "01"      => y <= X(1);
        WHEN OTHERS    => y <= X(2);
      END CASE;
    ELSE y <= '0';
    ENDIF;
  END PROCESS;
END ARCHITECTURE casestmt;
```




3:1 mux

e	s <sub>1</sub> s <sub>0</sub>	y
0	- -	0
1	0 0	x <sub>0</sub>
1	0 1	x <sub>1</sub>
1	1 0	x <sub>2</sub>
1	1 1	??


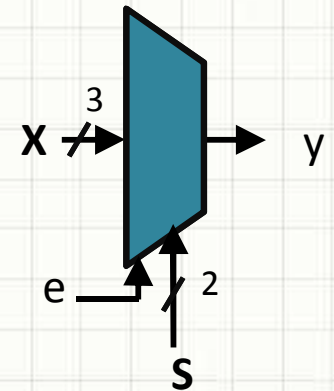
# Selected Signal Assignment

```
ARCHITECTURE ssa OF mux_3_1 IS
BEGIN
    SIGNAL t : bit;
    WITH S SELECT
        t <= X(0) WHEN "00",
            X(1) WHEN "01",
            X(2) WHEN OTHERS;
    y <= t AND e;
END ARCHITECTURE ssa;
```




3:1 mux

e	s <sub>1</sub> s <sub>0</sub>	y
0	- -	0
1	0 0	x <sub>0</sub>
1	0 1	x <sub>1</sub>
1	1 0	x <sub>2</sub>
1	1 1	??



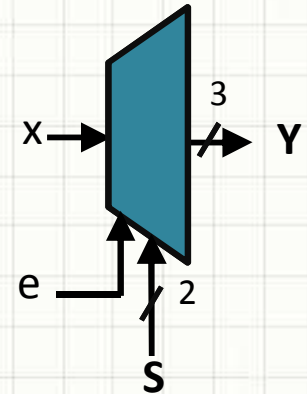
# 1 to 3 De-mux

```
ENTITY de-mux_1_3 IS
  PORT (x: IN    bit;
        e: IN    bit;
        S: IN    bit_vector (1 DOWNT0 0);
        Y: OUT   bit_vector (2 DOWNT0 0)
  );
END de-mux_1_3;
```


 
# CASE statement

```
ARCHITECTURE casestmt OF de-mux_1_3 IS
BEGIN
  PROCESS (S, x, e)
  BEGIN
    IF (x AND e) THEN
      CASE S IS
        WHEN "00"      => Y <= "001";
        WHEN "01"      => Y <= "010";
        WHEN OTHERS    => Y <= "100";
      END CASE;
    ELSE Y <= "000";
    ENDIF;
  END PROCESS;
END ARCHITECTURE casestmt;
```



1:3 de-mux

e	s <sub>1</sub> s <sub>0</sub>	Y <sub>2</sub> Y <sub>1</sub> Y <sub>0</sub>
0	- -	0 0 0
1	0 0	0 0 x
1	0 1	0 x 0
1	1 0	x 0 0
1	1 1	??

# Selected Signal Assignment

ARCHITECTURE ssa OF de-mux\_1\_3 IS  
BEGIN

SIGNAL T : bit\_vector (2 DOWNT0 0);

Y <= T WHEN (x AND e) ELSE

"000";


WITH S SELECT

T <= "001" WHEN "00",

"010" WHEN "01",

"100" WHEN OTHERS;

END ARCHITECTURE ssa;

 

1:3 de-mux

e	s <sub>1</sub> s <sub>0</sub>	Y <sub>2</sub> Y <sub>1</sub> Y <sub>0</sub>
0	- -	0 0 0
1	0 0	0 0 x
1	0 1	0 x 0
1	1 0	x 0 0
1	1 1	??

# 3 Input Priority Encoder

ENTITY Priority\_3 IS


PORT (X: IN bit\_vector (2 DOWNT0 0);

S: OUT bit\_vector (1 DOWNT0 0);

e: OUT bit

);

END Priority\_3;

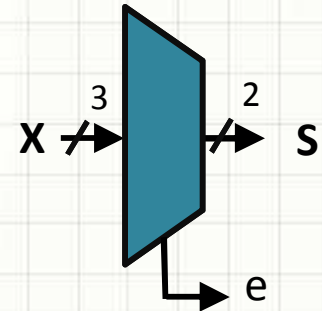

# IF statement

```
ARCHITECTURE ifstmt OF Priority_3 IS  
BEGIN
```

```
  PROCESS (X)
```

```
  BEGIN
```

```
    IF      X(2) = '1' THEN S <= "10"; e <= '1';
```

```
    ELSIF X(1) = '1' THEN S <= "01"; e <= '1';
```


```
    ELSIF X(0) = '1' THEN S <= "00"; e <= '1';
```

```
    ELSE                                S <= "00"; e <= '0';
```

```
  END IF;
```

```
  END PROCESS;
```

```
END ARCHITECTURE ifstmt;
```

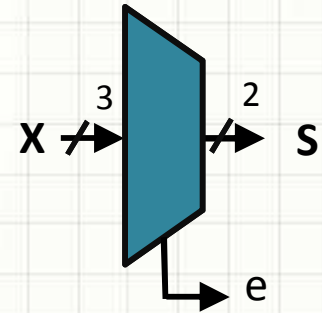

3 input priority encoder

$x_2x_1x_0$	$e \ s_1s_0$
0 0 0	0 - -
0 0 1	1 0 0
0 1 -	1 0 1
1 - -	1 1 0

# IF statement

ARCHITECTURE ifstmt OF Priority\_3 IS  
BEGIN

PROCESS (X)

BEGIN

IF X(2) = '1' THEN S <= "10";

ELSIF X(1) = '1' THEN S <= "01";

ELSE S <= "00";


END IF;

IF X = "000" THEN e <= '0'; ELSE e <= '1';

END IF;

END PROCESS;

END ARCHITECTURE ifstmt;

 

3 input priority encoder


$x_2x_1x_0$	$e \ s_1s_0$
0 0 0	0 - -
0 0 1	1 0 0
0 1 -	1 0 1
1 - -	1 1 0

# Conditional signal assignment

```
ARCHITECTURE cond OF Priority_3 IS  
BEGIN
```

```
    S <= "10" WHEN X(2) = '1' ELSE  
        "01" WHEN X(1) = '1' ELSE  
        "00";
```
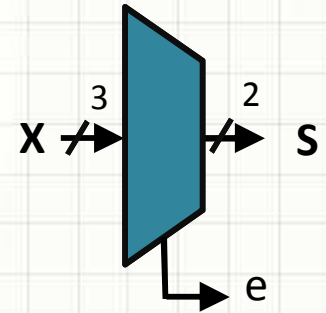
```
    e <= '0' WHEN X = "000" ELSE '1';  
END ARCHITECTURE cond;
```




3 input priority encoder

$x_2x_1x_0$	$e \ s_1s_0$
0 0 0	0 - -
0 0 1	1 0 0
0 1 -	1 0 1
1 - -	1 1 0



 
# 3 : 1 Mux, 2 bit wide

```
ENTITY mux_3_1_2bit IS
  PORT (X2: IN    bit_vector (1 DOWNT0 0);
        X1: IN    bit_vector (1 DOWNT0 0);
        X0: IN    bit_vector (1 DOWNT0 0);
        S: IN     bit_vector (1 DOWNT0 0);
        e: IN     bit;
        y: OUT bit_vector (1 DOWNT0 0)
  );
END mux_3_1_2bit;
```


 
# CASE statement

```
ARCHITECTURE casestmt OF mux_3_1_2bit IS
BEGIN
  PROCESS (S, X0, X1, X2, e)
  BEGIN
    IF e = '1' THEN
      CASE S IS
        WHEN "00"      => y <= X0;
        WHEN "01"      => y <= X1;
        WHEN OTHERS    => y <= X2;
      END CASE;
    ELSE y <= "00";
    ENDIF;
  END PROCESS;
END ARCHITECTURE casestmt;
```



3:1 mux

e	s <sub>1</sub> s <sub>0</sub>	y
0	- -	00
1	0 0	X0
1	0 1	X1
1	1 0	X2
1	1 1	??

# Selected Signal Assignment

ARCHITECTURE ssa OF mux\_3\_1\_2bit IS  
BEGIN


SIGNAL t : bit\_vector (1 DOWNTO 0);

WITH S SELECT

t <= X0 WHEN "00",  
X1 WHEN "01",  
X2 WHEN OTHERS;

y <= t AND e;

END ARCHITECTURE ssa;

 

3:1 mux

e	s <sub>1</sub> s <sub>0</sub>	y
0	- -	00
1	0 0	X0
1	0 1	X1
1	1 0	X2
1	1 1	??



**THANKS**