



COL215 DIGITAL LOGIC AND SYSTEM DESIGN

Designing with VHDL
Sequential Multiplier Design
12 September 2017

How to design using VHDL?

- Think in terms of VHDL constructs
- Any syntactically valid VHDL description is fine
- The tools should make correct sense out of it
- VHDL is just another programming language



How to design using VHDL?

- Think in terms of circuit structure
- Describe it in VHDL
- Use well understood abstractions
- Do not lose sight of underlying hardware



Design Styles

- An ARCHITECTURE can have -
 - Component instances (structural)
 - Processes (procedural)
 - Concurrent assignments (data flow)

These can be mixed but not advisable

- Structural hierarchy at the top
- Behavioural descriptions at the bottom

Semantics

- The whole design is a collection of concurrent processes
- Processes communicate with each other through signals
- No internal signals within processes, though the synthesizer may create some
- Ensure that each signal is driven by only one process (for the present)

What does a process mean?

- Repeated computation of values and assignment to signals
- A process executes in
 - zero time
 - non-zero time (not studied yet)
- A zero time process may represent
 - Either a combinational circuit
 - Or a Sequential circuit

Signals and processes

- A signal is either an output of a gate or a flip-flop (or an array of these)
- Driven by a process of appropriate type (combinational or sequential)
 - no mix up
 - no latches created by synthesizer
- Each signal driven by a unique process
- A process may drive multiple signals

Process describing a comb. circuit

- Sensitive to all its inputs
- Assigns to all outputs under all conditions

so that no latch is
created.

Process describing a sequential circuit

- Sensitive to a clock
- All assignments to outputs on clock edge
- Optionally, sensitive to additional signal(s)
- Use this only for initialization
- Initialization with declaration is good only for simulation
- Use DFF description as template

D Flip-flop with synch S/R

```
ARCHITECTURE synchronous OF DFFsr IS
BEGIN
  PROCESS (clk)
  BEGIN
    IF clk = '1' AND clk'EVENT THEN
      IF s = '1' THEN      q <= '1';
      ELSIF r = '1' THEN  q <= '0';
      ELSE                q <= d;
      END IF;
    END IF;
  END PROCESS;
END ARCHITECTURE synchronous;
```

D Flip-flop with asynch S/R

```
ARCHITECTURE asynchronous OF DFFsr IS  
BEGIN
```

```
    PROCESS (clk, s, r)
```

```
    BEGIN
```

```
        IF s = '1' THEN                                q <= '1';
```

```
        ELSIF r = '1' THEN                              q <= '0';
```

```
        ELSIF clk = '1' AND clk'EVENT THEN            q <= d;
```

```
    END IF;
```

```
    END PROCESS;
```

```
END ARCHITECTURE asynchronous;
```

Iteration in space / time

```
FOR i IN 0 TO 15 LOOP  
    sequential statements  
END LOOP
```

not studied yet

=> iteration in time

```
FOR i IN 0 TO 15 GENERATE  
    concurrent statements  
END GENERATE
```

=> iteration in space

Signal vs Variable

- Signals interconnect processes
- Variables are internal to processes
- A variable is updated instantly
- A signal is updated after a delay (the default is delta)




Serial arithmetic circuits

Parallel arithmetic circuits

Adders and Multipliers

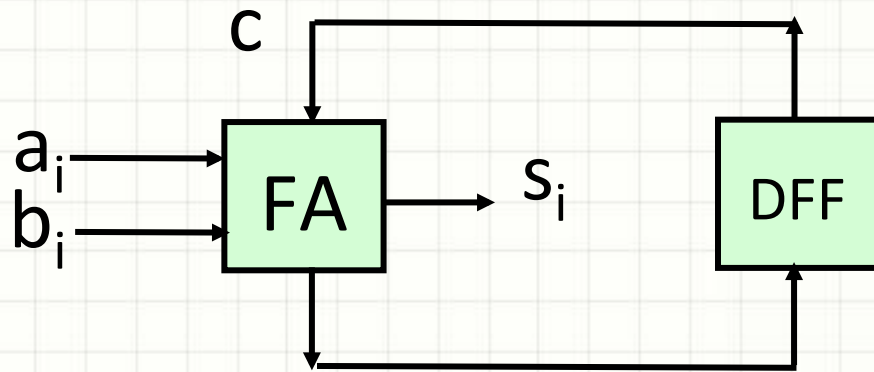- A serial adder can add two numbers of arbitrary size.



- Can a similar serial multiplier be designed?



Shift add multiplier (sequential)

$$A \times B = \sum_{i=0}^{n-1} A \cdot B_i \times 2^i$$

```
s = 0;  
for i in 0 to n - 1 loop  
    wait for clock edge;  
    s = s + A · Bi × 2i;  
end loop;
```

```
s = 0;  
for i in 0 to n - 1 loop  
    wait for clock edge;  
    s = s + A · Bi;  
    A = shift_left (A);  
end loop;
```

Shift-add multiply algorithm

shift s , rather than A

```
s = 0
for i in 0 to n-1 loop
  if ( $B_0$ ) then  $s = s + A$ 
end if
   $A = 2 \times A$ 
   $B = B / 2$ 
end loop
```

```
s = 0
for i in 0 to n-1 loop
  if ( $B_0$ ) then  $s_H = s_H + A$ 
end if
   $s = s / 2$ 
   $B = B / 2$ 
end loop
```


Shift-add multiply algorithm

place operand B in s


```
s = 0
for i in 0 to n-1 loop
  if ( $B_0$ ) then  $s_H = s_H + A$ 
end if
s = s / 2
B = B / 2
end loop
```

```
s = 0 | B
for i in 0 to n-1 loop
  if ( $s_0$ ) then  $s_H = s_H + A$ 
end if
s = s / 2
end loop
```


Sequential shift add multiplier 1

 

Sequential shift add multiplier 2

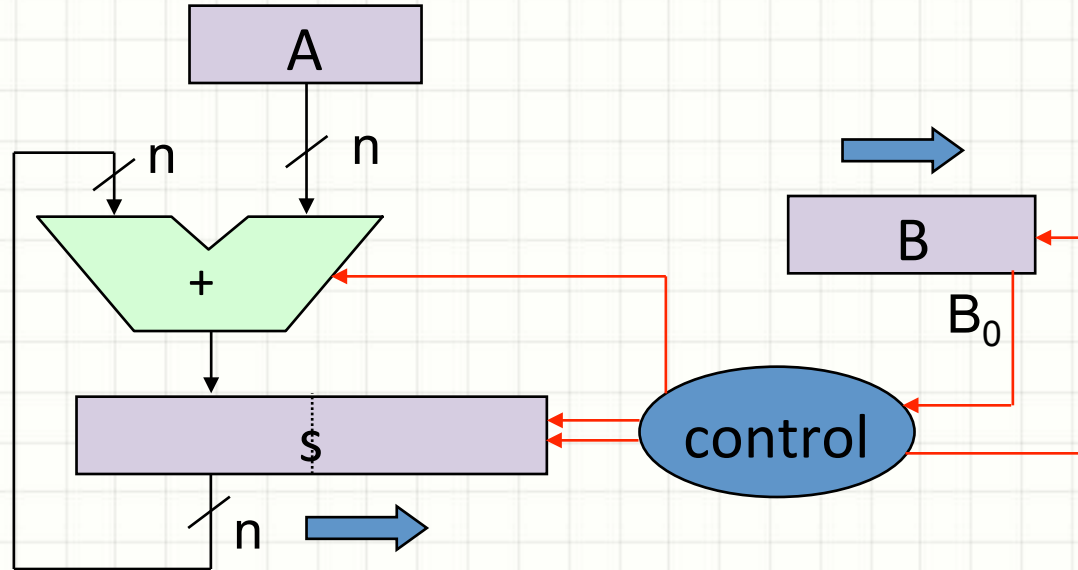


Sequential shift add multiplier 3

 


Shift-add multiply operation - 1

| A | S | B |
|----------|-------------|------|
| 00001011 | 00000000 | 1101 |
| | + 00001011 | |
| 0001011x | 00001011 | 0110 |
| | + 00000000x | |
| 001011xx | 00001011 | 0011 |
| | + 001011xx | |
| 01011xxx | 00110111 | 0001 |
| | + 01011xxx | |
| 1011xxxx | 10001111 | 0000 |

Shift-add multiply operation - 2

 

Shift-add multiply operation - 3

 



THANKS