



COL215 DIGITAL LOGIC AND SYSTEM DESIGN

- State Minimization in FSMs,
- Introduction to Asynchronous FSMs

07 November 2017



CUBICAL TECHNIQUE FOR MINIMIZATION

Star (*) operation

Possible results of operation

$C = A * B$ on cubes A and B

- if A and B are far apart, no new cube is generated
- if A, B overlap, the result is intersection of A and B
- if A, B differ in exactly one literal, new cube generated is union of a part of A and a part of B

$A_i \backslash B_i$	0	1	x
0	0	\emptyset	0
1	\emptyset	1	1
x	0	1	x

If $A_i * B_i = \emptyset$ for more than one i, then $C = \emptyset$

Otherwise, if $A_i * B_i \neq \emptyset$ then

$$C_i = A_i * B_i$$

else

$$C_i = x$$

Sharp (#) operation

Possible results of operation

$C = A \# B$ on cubes A and B

- if A and B are disjoint, the result is A
- if A is contained in B , the result is empty
- if B partly overlaps with A , the result is non-overlapping part of A

$A_i \setminus B_i$	0	1	x
0	ε	\emptyset	ε
1	\emptyset	ε	ε
x	1	0	ε

If $A_i \# B_i = \emptyset$ for some i ,
then $C = A$

If $A_i \# B_i = \varepsilon$ for all i ,
then $C = \emptyset$



STATE MINIMIZATION

Finite State Machine Model

Quintuple $(X, Y, S, \delta, \lambda)$

X = set of primary input patterns

Y = set of primary output patterns

S = set of states {includes an initial state}

δ = state transition function $S \times X \rightarrow S$

λ = output function

$S \times X \rightarrow Y$ for Mealy model or

$S \rightarrow Y$ for Moore model

Assumptions

- Synchronous circuits
- Single clock
- Single phase
- Edge triggered D type flip-flops/registers

Completely specified FSMs

Definition of state equivalence:

$\text{equiv}(s_i, s_j)$ iff

$\text{output_seq}(s_i, \text{input_seq}) =$
 $\text{output_seq}(s_j, \text{input_seq})$

for all input_seq

Incompletely specified FSMs

- Definition of compatible states:

$\text{comp}(s_i, s_j)$ iff
 $\text{output_seq}(s_i, \text{input_seq}) =$
 $\text{output_seq}(s_j, \text{input_seq})$
when *both are defined*,

for all *applicable* input_seq

Incompletely specified FSMs

- Easier way to check compatibility:

$\text{comp}(s_i, s_j) \equiv$

$(s_i = s_j)$

or

$\lambda(s_i, x) = \lambda(s_j, x)$ *if both are defined* and

$\text{comp}(\delta(s_i, x), \delta(s_j, x)),$

for all *applicable* x in X

Equivalence vs compatibility

- Reflexive, symmetric and transitive
- Equivalence classes (groups of equivalent states) are disjoint
- Partition is unique
- Reflexive, symmetric but NOT transitive
- Compatibility classes (groups of compatible states) are overlapping
- Partition is not unique, each choice has “implications”

“Implications” while partitioning

- If states A and B are chosen as compatible, successor of A and successor of B (*under all applicable inputs*) should also be chosen as compatible
- **Closure property:** A partition has closure property if all the implications are taken care of

Example

In	PS	NS	Out
0	s_1	s_3	1
1	s_1	s_5	*
0	s_2	s_3	*
1	s_2	s_5	1
0	s_3	s_2	0
1	s_3	s_1	1
0	s_4	s_4	0
1	s_4	s_5	1
0	s_5	s_4	1
1	s_5	s_1	0


There is an exponential number of completely specified FSMs corresponding to an incompletely specified FSM

Compatible pairs

	Pairs	Depends on
Compatible	$\{s_1, s_2\}$	
Compatible	$\{s_1, s_5\}$	$\{s_3, s_4\}$
Compatible	$\{s_2, s_4\}$	$\{s_3, s_4\}$
Compatible	$\{s_2, s_3\}$	$\{s_1, s_5\}$
Compatible	$\{s_3, s_4\}$	$\{s_2, s_4\}, \{s_1, s_5\}$
Incompatible	$\{s_1, s_3\}$	
Incompatible	$\{s_1, s_4\}$	
Incompatible	$\{s_2, s_5\}$	
Incompatible	$\{s_3, s_5\}$	
Incompatible	$\{s_4, s_5\}$	

In	PS	NS	Out
0	s_1	s_3	1
1	s_1	s_5	*
0	s_2	s_3	*
1	s_2	s_5	1
0	s_3	s_2	0
1	s_3	s_1	1
0	s_4	s_4	0
1	s_4	s_5	1
0	s_5	s_4	1
1	s_5	s_1	0

Compatibility classes

 

Classes

Implied
classes

$\{s_1, s_2\}$

$\{s_1, s_5\}$

$\{s_2, s_3, s_4\}$

$\{s_3, s_4\}$


$\{s_1, s_5\}$

Selected classes may not
always be maximal

Minimized FSM Table


In	PS	NS	Out
0	s ₁	s ₃	1
1	s ₁	s ₅	*
0	s ₂	s ₃	*
1	s ₂	s ₅	1
0	s ₃	s ₂	0
1	s ₃	s ₁	1
0	s ₄	s ₄	0
1	s ₄	s ₅	1
0	s ₅	s ₄	1
1	s ₅	s ₁	0

In	PS	NS	Out
0	s ₁₅	s ₂₃₄	1
1	s ₁₅	s ₁₅	0
0	s ₂₃₄	s ₂₃₄	0
1	s ₂₃₄	s ₁₅	1

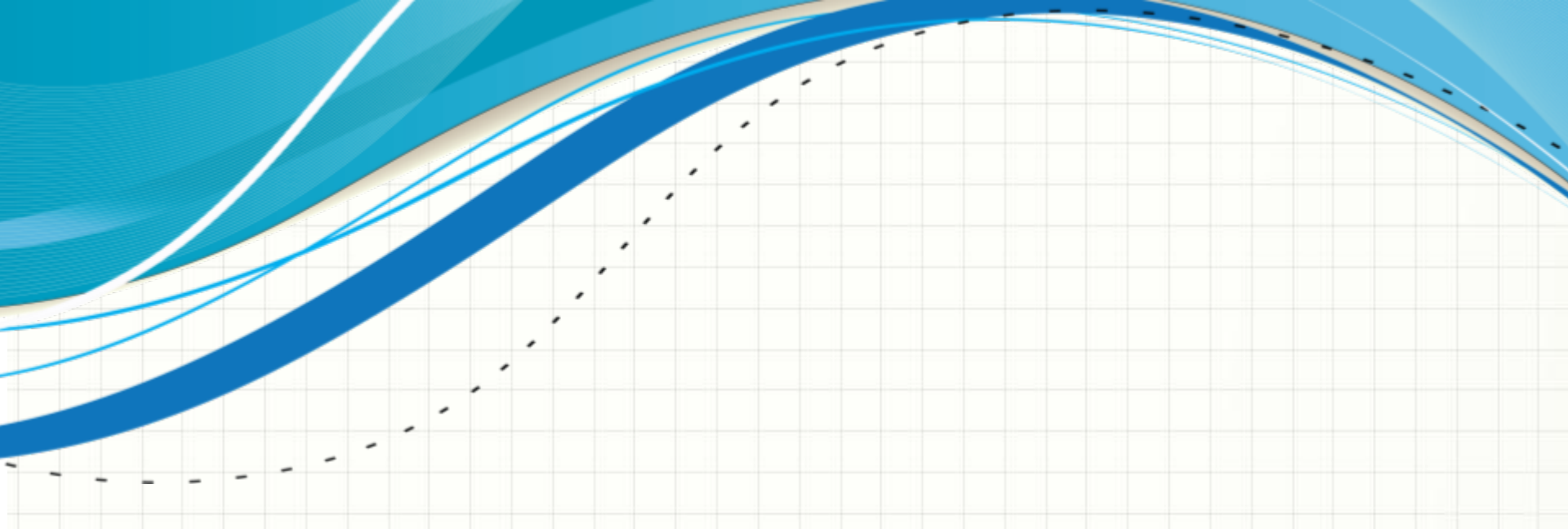


INTRODUCTION TO ASYNCHRONOUS FSMs


Synchronous FSM (Moore)

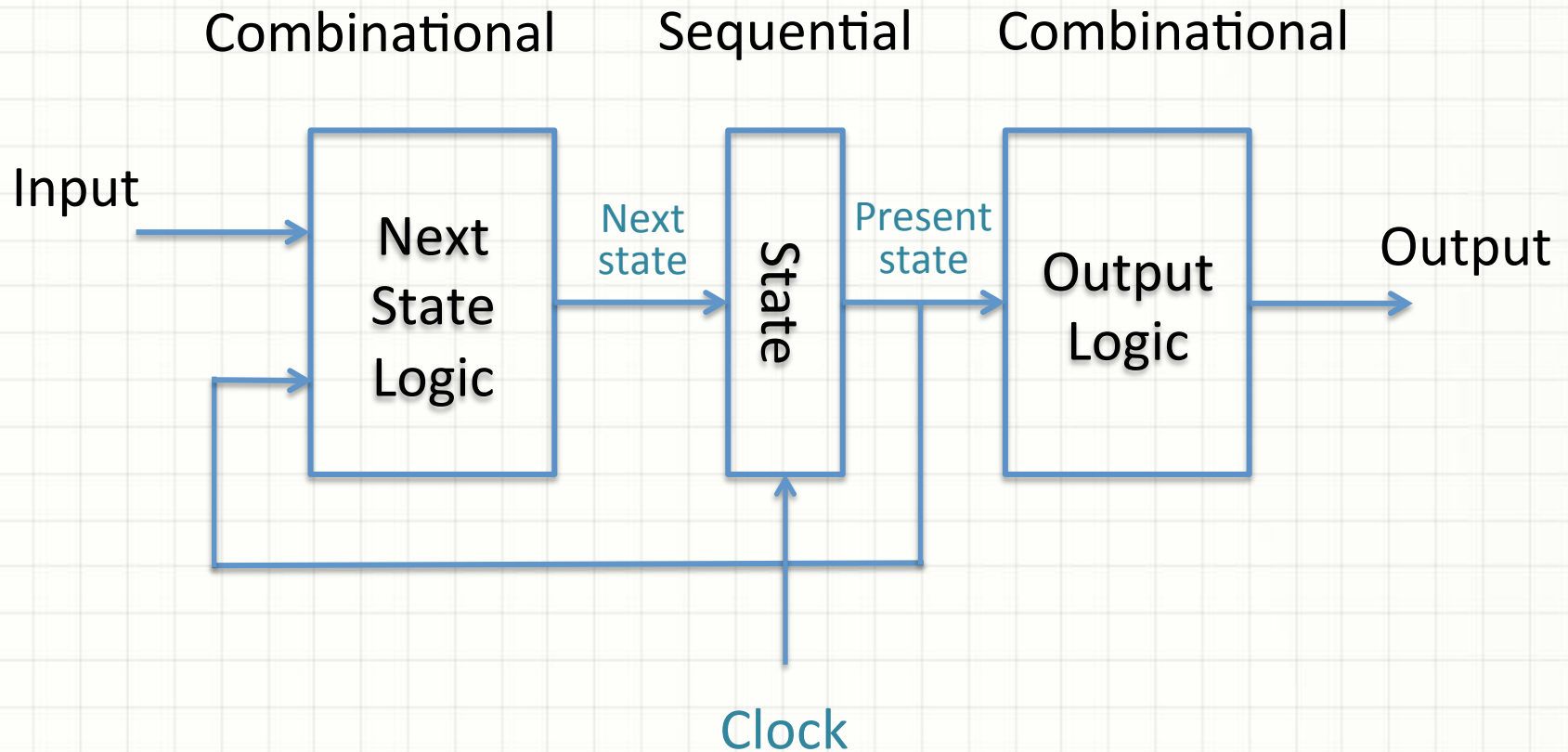

Synchronous FSM (Mealy)

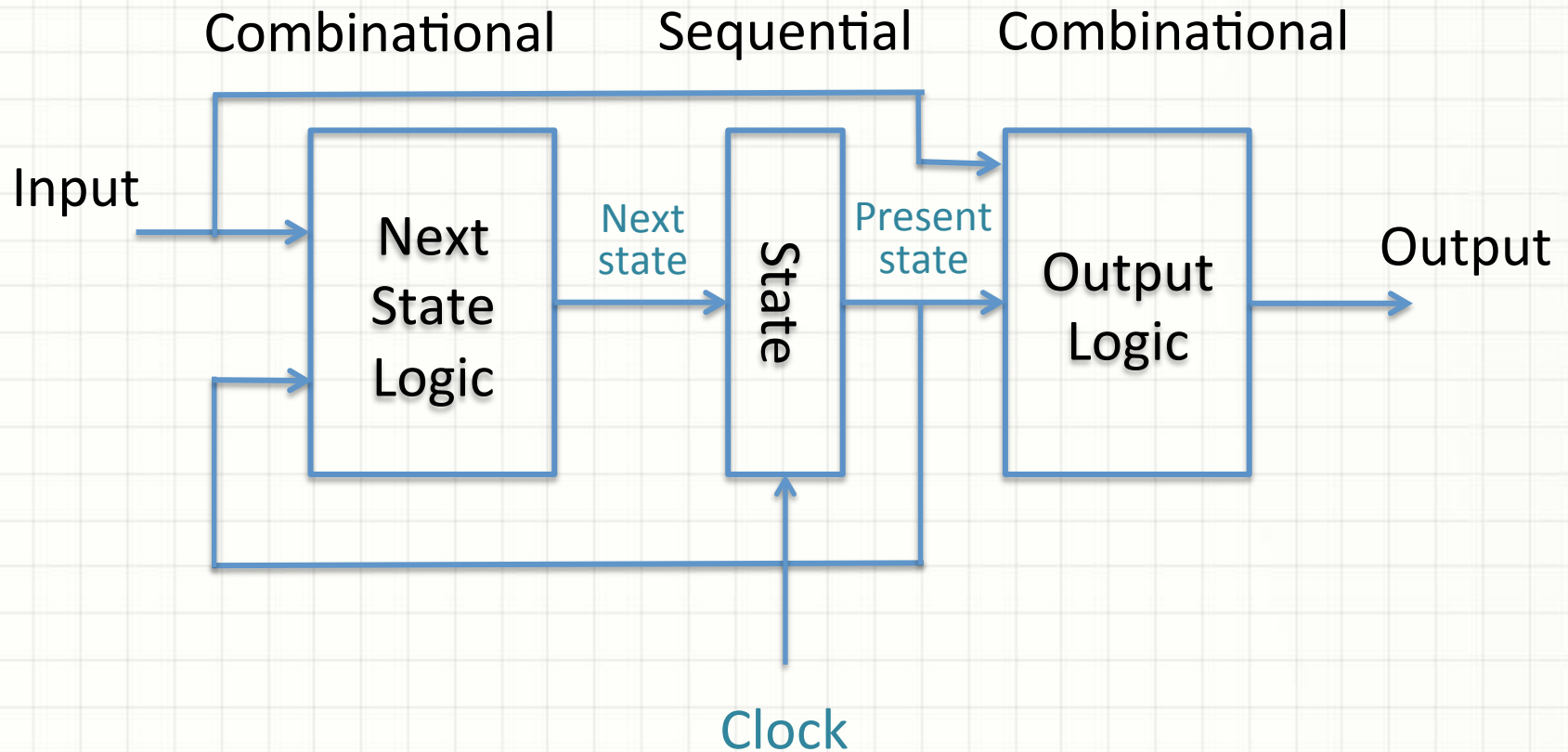


Asynchronous FSM (Mealy)

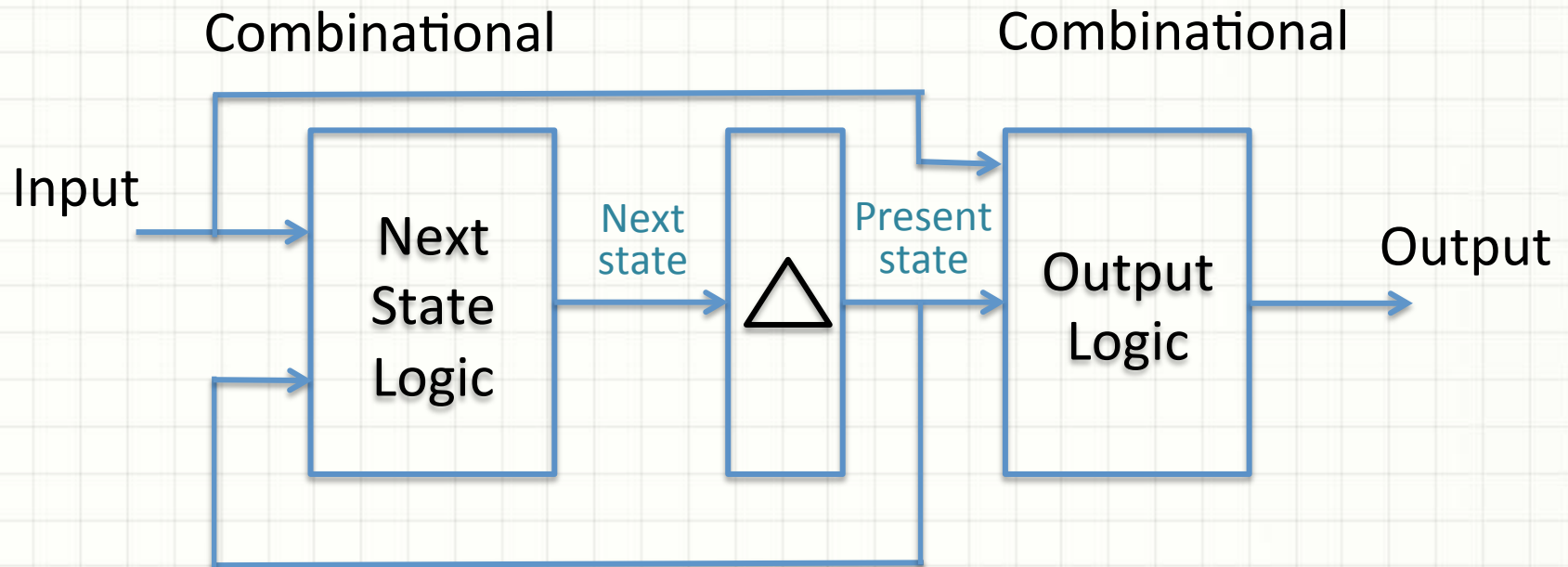

Outline

- SR Latch
- Gated D Latch
- Master-Slave D Flip-flop


Set-Reset (SR) Latch

 

R : Reset

S : Set


Set-Reset (SR) Latch

 

R : Reset


S : Set

State assigned table

 

$$Y = ((S + y)' + R)' = (S + y).R' = S.R' + y.R'$$


State assigned table

 

Present state y	Next state Y				Output Q
	SR = 00	SR = 01	SR = 10	SR = 11	
0	0	0	1	0	0
1	1	0	1	0	1

$$Y = ((S + y)' + R)' = (S + y).R' = S.R' + y.R'$$


State assigned table

 

Present state y	Next state Y				Output Q
	SR = 00	SR = 01	SR = 10	SR = 11	
0	0	0	1	0	0
1	1	0	1	0	1

○ stable state


State transition table

 

Present state y	Next state Y				Output Q
	SR = 00	SR = 01	SR = 10	SR = 11	
A	A	A	B	A	0
B	B	A	B	A	1


State transition diagram

Present state y	Next state Y				Output Q
	SR = 00	SR = 01	SR = 10	SR = 11	
A	A	A	B	A	0
B	B	A	B	A	1

 

State transition diagram

Present state y	Next state Y				Output Q
	$SR = 00$	$SR = 01$	$SR = 10$	$SR = 11$	
A	A	A	B	A	0
B	B	A	B	A	1

 



QUESTIONS?