

1. 2's complement of an n -bit binary number $B = b_{n-1} b_{n-2} \dots b_1 b_0$ is given by

- (a) $b'_{n-1} b'_{n-2} \dots b'_{k+1} b_k b_{k-1} \dots b_1 b_0$, where b_k is the rightmost 0 in B . \times
(b) $b'_{n-1} b'_{n-2} \dots b'_{k+1} b_k b_{k-1} \dots b_1 b_0$, where b_k is the rightmost 1 in B . \checkmark
(c) $b_{n-1} b_{n-2} \dots b_{k+1} b'_k b'_{k-1} \dots b'_1 b'_0$, where b_k is the rightmost 0 in B .
(d) $b_{n-1} b_{n-2} \dots b_{k+1} b'_k b'_{k-1} \dots b'_1 b'_0$, where b_k is the rightmost 1 in B .

Which one of the above is correct? Give a proof. Here b_0 is the least significant bit.

[2]

2. Consider the algorithm given below for dividing 16 bit unsigned Dividend by 16 bit unsigned Divisor. The Quotient and Remainder are also 16 bit. R and D are 32 bit integers, R is signed and D is unsigned. Give a VHDL implementation of this algorithm such that it takes 18 clock cycles – one cycle for each iteration of the loop and one cycle each for the initialization step and the final step. Do not use variables, LOOP, WAIT and AFTER.

Initialization step: $R = \text{Dividend}$; $Q = 0$; $D = \text{Divisor} \times 2^{n-1}$


$n=16$

Loop: for $i = 0$ to 15 do {
 if $(R < 0)$ $R = R + D$ else $R = R - D$
 $Q = 2 \times Q + s$ where s is the sign bit of adder/subtractor output
 $D = D / 2$


}
Final step: if $(R < 0)$ Remainder = $R + \overset{\text{Divisor}}{D}$ else Remainder = R
 Quotient = Q

[3]

 3. What logic gate is realized by the circuit shown? Does the circuit suffer from any major drawbacks? Give reasons for your answer.



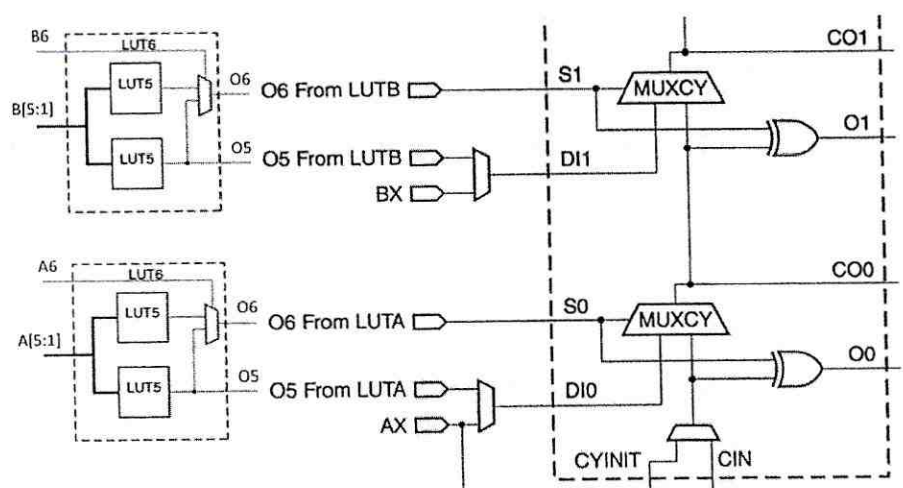4. The figure shows a part of a slice of Spartan 6 series FPGAs. On the right side, a portion of the carry chain circuit (2 bits out of 4) is shown and on the left side, two of the 6-input LUTs are shown. Note that each 6-input LUT consists of two 5-input LUTs. What logic functions should be implemented by the LUTs shown to make a 2-bit portion of a fast carry propagate adder?



[2]

A1) Let $C = (2's \text{ complement of } B)$

$$\Rightarrow C = \bar{B} + 1$$

$$\bar{B} = b'_{m-1} b'_{m-2} \dots b'_k b'_{k-1} \dots b'_1 b'_0$$

Adding 1 to a bit, inverts the bit. Also, a carry is generated only if the original bit was 1. Hence, on adding 1 to a bit that is 1 will continue the chain while adding 1 to a bit that is 0 will terminate the chain. So this chain continues only till the first 0 is encountered from right. That bit would have been 1 before in B as we are adding 1 to \bar{B} .

Let b_k be the rightmost 1 in B.
So all bits to right of b_k are 0.

$$\Rightarrow B = b_{m-1} b_{m-2} \dots b_{k+1} \underbrace{000 \dots 0}_{k \text{ bits}}$$

$$\bar{B} = b'_{m-1} b'_{m-2} \dots b'_{k+1} \underbrace{0111 \dots 1}_{k \text{ bits}}$$

$$\bar{B} = \sum_{i=k+1}^{m-1} b'_i 2^i + \sum_{i=0}^{k-1} 2^i = \sum_{i=k+1}^{m-1} b'_i 2^i + 2^k - 1$$

$$\bar{B} + 1 = \sum_{i=k+1}^{m-1} b'_i 2^i + 2^k$$

$$\bar{B} + 1 = b'_{m-1} b'_{m-2} \dots b'_{k+1} \underbrace{1000 \dots 0}_{k \text{ bits}}$$

$$\bar{B} + 1 = b'_{m-1} b'_{m-2} \dots b'_{k+1} b_k b_{k-1} \dots b_1 b_0$$

Hence option B is correct.

Sheet 1

(Samarth Aggarwal)
2016 CS10395

A2) use IEEE

entity divisor is

~~port (dividend, divisor : in integer;~~

port (dividend, divisor : in integer; clk : in bit;
quotient, remainder : out bit_vectors (16 downto 0));

end divisor

architecture arc of divisor is

signal x : ~~integer~~ integer;

signal d : integer;

signal x1 : bit_vector (31 downto 0)

signal d1 : bit_vector (31 downto 0)

signal q : bit_vector (15 downto 0)

begin

process (clk, dividend, divisor)

begin

if clk'event and clk='1' then

if dividend'event or divisor'event then

x ← dividend;

d ← divisor;

q ← "0000000000000000";

x1 ← q & q;

d1 ← q & d;

for i in 0 to 15 generate

x1 ← x1 + (x mod 2);

x ← x/2;

d1 ← d1 + (d mod 2);

d ← d/2;

end generate

q ≤ d (15 downto 0) & "0000000000000000";

end if

else then

A3) ~~The~~ $y = \bar{a}b + a\bar{b}$


The XOR logic gate is realised because when $a=1$, the NMOS transistor is turned on and it connects y to output of ~~the~~ CMOS inverter. When $a=0$, PMOS transistor is on and it connects y to b .

This circuit suffers a major drawback in 2 cases:-

I) When $a=1, b=0 \Rightarrow$ In this case, the NMOS transistor is used to pass 1 to the other side which the NMOS does ~~not do~~ with a drop. So here y will be $(V_{dd} - V_T)$ where V_T is the threshold voltage of NMOS.

II) When $a=0, b=0, \Rightarrow$ Here PMOS transistor is used to pass a 0 to the other side. Since PMOS ~~passes~~ ~~and~~ does not pass 0 efficiently hence this is drawback. y will attain the value V_T here as the PMOS turns off if y goes below that value.

A3) $f = x_1 \bar{x}_2 + \bar{x}_1 x_2$

 

LUTs should implement

A4) $f = x_1 x_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + \bar{x}_1 x_2 \bar{x}_3 + \bar{x}_1 \bar{x}_2 x_3$

LUT 1 should implement $(x_1 \oplus x_2 \oplus x_3)$

& LUT 2 should implement $(x_1 x_2 + x_2 x_3 + x_3 x_1)$.