



COL215 DIGITAL LOGIC AND SYSTEM DESIGN

Designing synchronous
sequential circuits

25 August 2016



Outline


- Saturating up/down counter
- Arbiter example
- FSMs in VHDL
- Moore and Mealy models

Saturating up-down counter

Design a synchronous up-down counter with the following specifications

- It has one input w and one 3-bit output Z
- Output Z is the count
- Input w decides whether count goes up ($w = 1$) or down ($w = 0$)
- The count saturates at 0 while counting down and at 5 while counting up.
- Initially, the count is 0

State transition diagram

 

State transition table

Present state	Next state		Output z
	w = 0	w = 1	
S_0	S_0	S_1	0 0 0
S_1	S_0	S_2	0 0 1
S_2	S_1	S_3	0 1 0
S_3	S_2	S_4	0 1 1
S_4	S_3	S_5	1 0 0
S_5	S_4	S_5	1 0 1

State transition table

state encoding is trivial here

Present state	Next state		Output z
	w = 0	w = 1	
0 0 0	0 0 0	0 0 1	0 0 0
0 0 1	0 0 0	0 1 0	0 0 1
0 1 0	0 0 1	0 1 1	0 1 0
0 1 1	0 1 0	1 0 0	0 1 1
1 0 0	0 1 1	1 0 1	1 0 0
1 0 1	1 0 0	1 0 1	1 0 1

present state = $y_2 y_1 y_0$

next state = $Y_2 Y_1 Y_0$

output = $z_2 z_1 z_0$

= $y_2 y_1 y_0$

Implementation using D FFs

$y_2 y_1 y_0$	Y_2	
	w'	w
0 0 0	0	0
0 0 1	0	0
0 1 0	0	0
0 1 1	0	1
1 0 0	0	1
1 0 1	1	1

$y_2 y_1 y_0$	Y_1	
	w'	w
0 0 0	0	0
0 0 1	0	1
0 1 0	0	1
0 1 1	1	0
1 0 0	1	0
1 0 1	0	0

$y_2 y_1 y_0$	Y_0	
	w'	w
0 0 0	0	1
0 0 1	0	0
0 1 0	1	1
0 1 1	0	0
1 0 0	1	1
1 0 1	0	1

$$Y_2 = y_2 y_1' y_0 + w y_2 y_1' + w y_2' y_1 y_0$$

$$Y_1 = w' y_2 y_1' y_0' + w' y_2' y_1 y_0 + w y_2' y_1 y_0' + w y_2' y_1' y_0$$

$$Y_0 = y_2 y_1' y_0' + y_2' y_1 y_0' + w y_2 y_1' + w y_2' y_0'$$

Implementation using T FFs

$y_2 y_1 y_0$	T_2	
	w'	w
000	0	0
001	0	0
010	0	0
011	0	1
100	1	0
101	0	0

$y_2 y_1 y_0$	T_1	
	w'	w
000	0	0
001	0	1
010	1	0
011	0	1
100	1	0
101	0	0

$y_2 y_1 y_0$	T_0	
	w'	w
000	0	1
001	1	1
010	1	1
011	1	1
100	1	1
101	1	0

$$T_2 = w' y_2 y_1' y_0' + w y_2' y_1 y_0$$

$$T_1 = w' y_2 y_1' y_0' + w' y_2' y_1 y_0' + w y_2' y_0$$

$$T_0 = y_2' y_0 + y_2' y_1 + w' y_2 y_1' + w y_1' y_0'$$

Implementation using JK FFs

$y_2 y_1 y_0$	$J_2 K_2$	
	w'	w
0 0 0	0 -	0 -
0 0 1	0 -	0 -
0 1 0	0 -	0 -
0 1 1	0 -	1 -
1 0 0	- 1	- 0
1 0 1	- 0	- 0

$y_2 y_1 y_0$	$J_1 K_1$	
	w'	w
0 0 0	0 -	0 -
0 0 1	0 -	1 -
0 1 0	- 1	- 0
0 1 1	- 0	- 1
1 0 0	1 -	0 -
1 0 1	0 -	0 -

$y_2 y_1 y_0$	$J_0 K_0$	
	w'	w
0 0 0	0 -	1 -
0 0 1	- 1	- 1
0 1 0	1 -	1 -
0 1 1	- 1	- 1
1 0 0	1 -	1 -
1 0 1	- 1	- 0

$$J_2 = w y_2' y_1 y_0$$

$$J_1 = w' y_2 y_1' y_0' + w y_2' y_0$$

$$J_0 = w y_2' + y_2 y_1' + y_2' y_1$$

$$K_2 = w' y_1' y_0'$$

$$K_1 = w' y_2' y_0' + w y_2' y_0$$

$$K_0 = y_2' + w' y_1'$$

D FF implementation with don't cares

$y_2 y_1 y_0$	Y_2	
	w'	w
0 0 0	0	0
0 0 1	0	0
0 1 0	0	0
0 1 1	0	1
1 0 0	0	1
1 0 1	1	1
1 1 0	-	-
1 1 1	-	-

$y_2 y_1 y_0$	Y_1	
	w'	w
0 0 0	0	0
0 0 1	0	1
0 1 0	0	1
0 1 1	1	0
1 0 0	1	0
1 0 1	0	0
1 1 0	-	-
1 1 1	-	-

$y_2 y_1 y_0$	Y_0	
	w'	w
0 0 0	0	1
0 0 1	0	0
0 1 0	1	1
0 1 1	0	0
1 0 0	1	1
1 0 1	0	1
1 1 0	-	-
1 1 1	-	-

$$Y_2 = y_2 y_0 + w y_2 + w y_1 y_0$$

$$Y_1 = w' y_2 y_0' + w' y_1 y_0 + w y_1 y_0' + w y_2' y_1' y_0$$

$$Y_0 = y_2 y_0' + y_1 y_0' + w y_2 + w y_0'$$

T FF implementation with don't cares

$y_2 y_1 y_0$	T_2	
	w'	w
0 0 0	0	0
0 0 1	0	0
0 1 0	0	0
0 1 1	0	1
1 0 0	1	0
1 0 1	0	0
1 1 0	-	-
1 1 1	-	-

$y_2 y_1 y_0$	T_1	
	w'	w
0 0 0	0	0
0 0 1	0	1
0 1 0	1	0
0 1 1	0	1
1 0 0	1	0
1 0 1	0	0
1 1 0	-	-
1 1 1	-	-

$y_2 y_1 y_0$	T_0	
	w'	w
0 0 0	0	1
0 0 1	1	1
0 1 0	1	1
0 1 1	1	1
1 0 0	1	1
1 0 1	1	0
1 1 0	-	-
1 1 1	-	-

$$T_2 = w' y_2 y_0' + w y_1 y_0$$

$$T_1 = w' y_2 y_0' + w' y_1 y_0' + w y_2' y_0$$

$$T_0 = y_2' y_0 + y_2' y_1 + w' y_2 + w y_0'$$

JK FF implementation with don't cares

$y_2 y_1 y_0$	$J_2 K_2$	
	w'	w
0 0 0	0 -	0 -
0 0 1	0 -	0 -
0 1 0	0 -	0 -
0 1 1	0 -	1 -
1 0 0	- 1	- 0
1 0 1	- 0	- 0
1 1 0	- -	- -
1 1 1	- -	- -

$y_2 y_1 y_0$	$J_1 K_1$	
	w'	w
0 0 0	0 -	0 -
0 0 1	0 -	1 -
0 1 0	- 1	- 0
0 1 1	- 0	- 1
1 0 0	1 -	0 -
1 0 1	0 -	0 -
1 1 0	- -	- -
1 1 1	- -	- -

$y_2 y_1 y_0$	$J_0 K_0$	
	w'	w
0 0 0	0 -	1 -
0 0 1	- 1	- 1
0 1 0	1 -	1 -
0 1 1	- 1	- 1
1 0 0	1 -	1 -
1 0 1	- 1	- 0
1 1 0	- -	- -
1 1 1	- -	- -

$$J_2 = w y_1 y_0$$

$$J_1 = w' y_2 y_0' + w y_2' y_0$$

$$J_0 = w + y_2 + y_1$$

$$K_2 = w' y_0'$$

$$K_1 = w' y_0' + w y_0$$

$$K_0 = y_2' + w'$$

What about states “110” and “111”?

$y_2 y_1 y_0$	Y_2	
	w'	w
0 0 0	0	0
0 0 1	0	0
0 1 0	0	0
0 1 1	0	1
1 0 0	0	1
1 0 1	1	1
1 1 0	0	1
1 1 1	1	1

$y_2 y_1 y_0$	Y_1	
	w'	w
0 0 0	0	0
0 0 1	0	1
0 1 0	0	1
0 1 1	1	0
1 0 0	1	0
1 0 1	0	0
1 1 0	1	1
1 1 1	1	0

$y_2 y_1 y_0$	Y_0	
	w'	w
0 0 0	0	1
0 0 1	0	0
0 1 0	1	1
0 1 1	0	0
1 0 0	1	1
1 0 1	0	1
1 1 0	1	1
1 1 1	0	1

$$Y_2 = y_2 y_0 + w y_2 + w y_1 y_0$$


$$Y_1 = w' y_2 y_0' + w' y_1 y_0 + w y_1 y_0' + w y_2' y_1' y_0$$

$$Y_0 = y_2 y_0' + y_1 y_0' + w y_2 + w y_0'$$

State transition table

Present state	Next state		Output z
	w = 0	w = 1	
0 0 0	0 0 0	0 0 1	0 0 0
0 0 1	0 0 0	0 1 0	0 0 1
0 1 0	0 0 1	0 1 1	0 1 0
0 1 1	0 1 0	1 0 0	0 1 1
1 0 0	0 1 1	1 0 1	1 0 0
1 0 1	1 0 0	1 0 1	1 0 1
1 1 0	0 1 1	1 1 1	1 1 0
1 1 1	1 1 0	1 0 1	1 1 1

State transition diagram

 

Revisiting arbiter of 3 port switch


Previous design :

- Arbitration done by priority encoder
- Fixed priorities
- Connections through low priority ports get interrupted


Improved design :

- Prevents interruption
- It remembers which port is already communicating
- Sequential circuit rather than combinational

Arbiter

 

State transition diagram

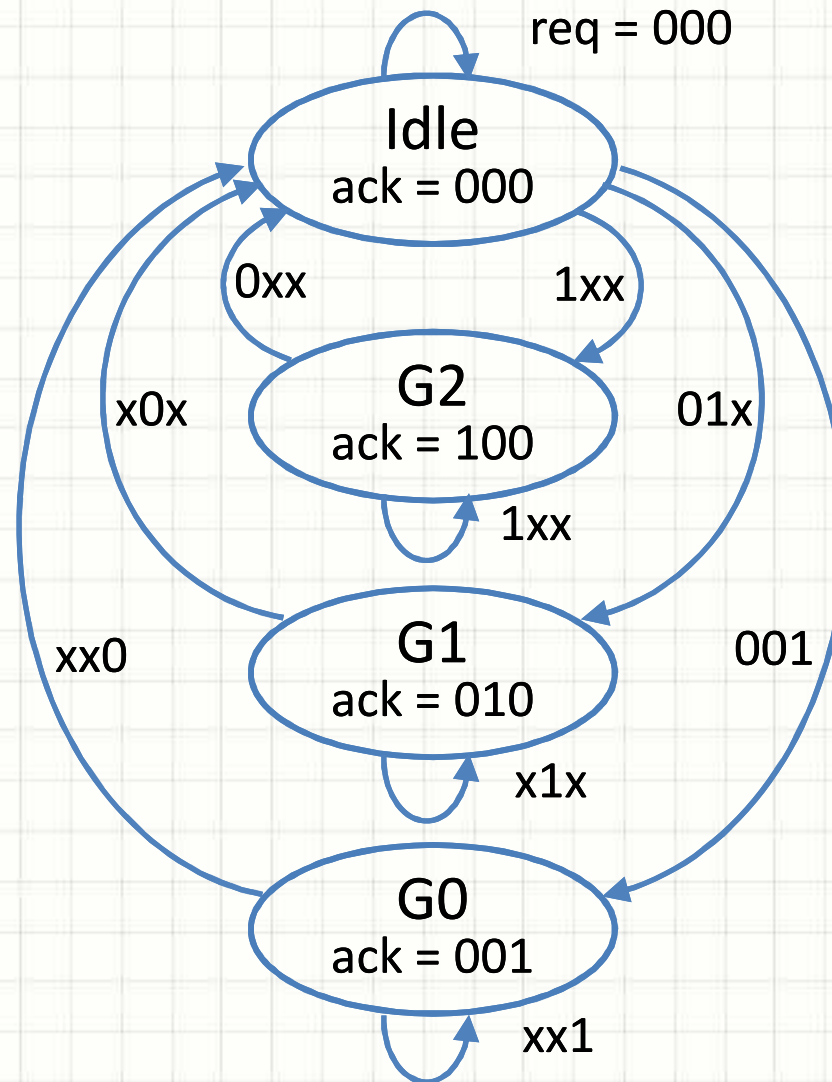

Design in VHDL - entity

```
ENTITY arbiter IS
```

```
    PORT (clk : IN bit;
```

```
          req : IN bit_vector (2 DOWNT0 0);
```

```
          ack : OUT bit_vector (2 DOWNT0 0)
```

```
    );
```

```
END arbiter;
```

Design in VHDL - architecture

ARCHITECTURE FSM OF arbiter IS

TYPE state_type IS (Idle, G0, G1, G2);

SIGNAL state : state_type;

BEGIN

PROCESS (clk)

... define next state here

END PROCESS;

WITH state SELECT

... define output here

END FSM;

Next state process

```
PROCESS (clk)
BEGIN
    IF clk'EVENT AND clk = '1' THEN
        CASE state IS
            WHEN Idle => ...
            WHEN G2 => ...
            WHEN G1 => ...
            WHEN Go => ...
        END CASE;
    END IF;
END PROCESS;
```

Case statement

CASE state IS

 WHEN Idle =>

 IF req (2) = '1' THEN state <= G2;

 ELSIF req (1) = '1' THEN state <= G1;

 ELSIF req (0) = '1' THEN state <= G0;

 END IF;

 WHEN G2 =>

 IF req (2) = '0' THEN state <= Idle; END IF;

 WHEN G1 =>

 IF req (1) = '0' THEN state <= Idle; END IF;

 WHEN G0 =>

 IF req (0) = '0' THEN state <= Idle; END IF;

END CASE;

Selected signal assignment

WITH state SELECT

```
ack <= "000"  WHEN Idle ,  
      "100"  WHEN G2 ,  
      "010"  WHEN G1 ,  
      "001"  WHEN G0;
```


Next state and output together

CASE state IS

WHEN Idle =>

IF req (2) = '1' THEN ack <= "100"; state <= G2;

ELSIF req (1) = '1' THEN ack <= "010"; state <= G1;

ELSIF req (0) = '1' THEN ack <= "001"; state <= G0;

ELSE
ack <= "000"; END IF;

WHEN G2 =>

IF req (2) = '0' THEN ack <= "000"; state <= Idle;

ELSE
ack <= "100"; END IF;

WHEN G1 =>

IF req (1) = '0' ...

WHEN G0 =>

IF req (0) = '0' ...

END CASE;



Moore and Mealy models


Moore

- Output is a function of present state only

Mealy


- Output is a function of present state as well as inputs

Moore FSM example

 


Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	D	C	1
D	A	C	1

Mealy FSM example

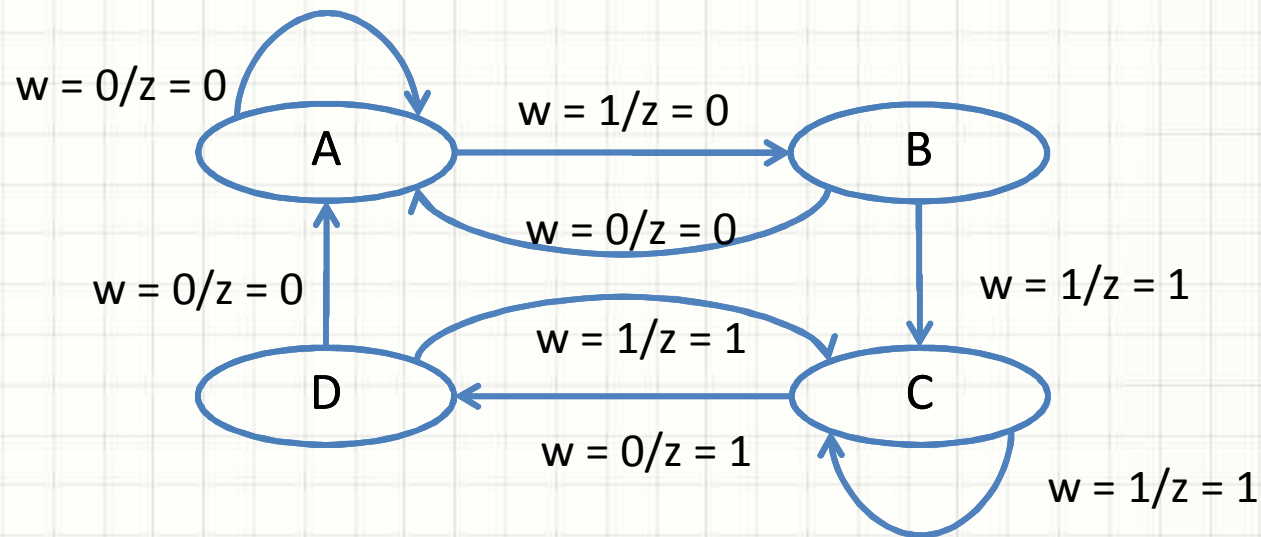

Present state	Next state/Output z	
	w = 0	w = 1
A	A/0	B/0
B	A/0	C/1
C	D/1	C/1
D	A/0	C/1

Circuit structure for Mealy FSM

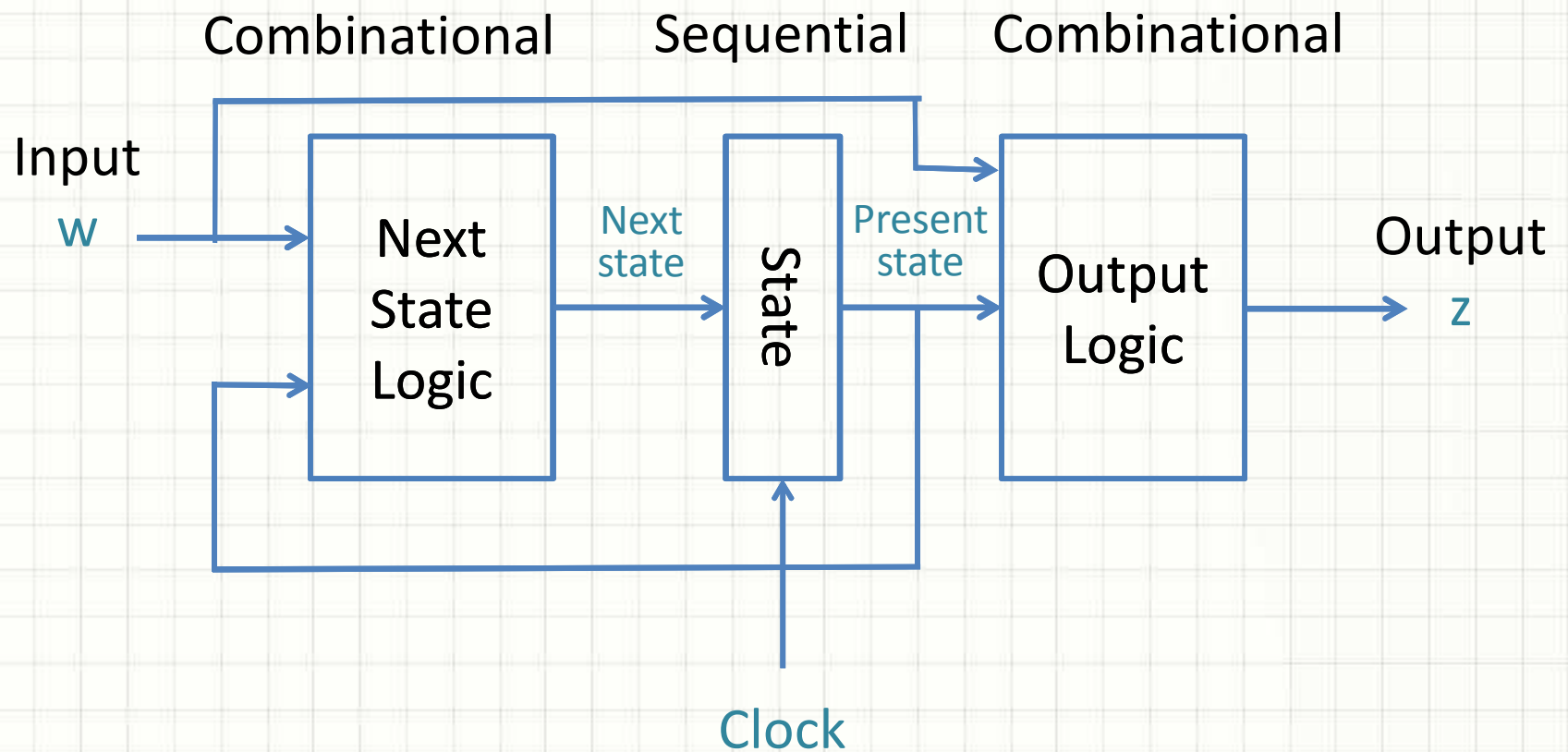

Next state for Moore/Mealy

CASE state IS

WHEN A =>

IF w = '1' THEN state <= B; END IF;

WHEN B =>

IF w = '1' THEN state <= C; ELSE state <= A; END IF;

WHEN C =>

IF w = '0' THEN state <= D; END IF;

WHEN D =>

IF w = '0' THEN state <= A; ELSE state <= C; END IF;

END CASE;

Output for Moore FSM

WITH state SELECT

```
z <= '0' WHEN A ,  
      '0' WHEN B ,  
      '1' WHEN C ,  
      '1' WHEN D;
```

Output for Mealy FSM

CASE state IS

WHEN A =>

z <= '0';

WHEN B =>

IF w = '1' THEN z <= '1'; ELSE z <= '0'; END IF;

WHEN C =>

z <= '1';

WHEN D =>

IF w = '0' THEN z <= '0'; ELSE z <= '1'; END IF;

END CASE;

Mealy FSM output – another way

```
CASE state IS  
  WHEN A =>  
    z <= '0';  
  WHEN B =>  
    z <= w;  
  WHEN C =>  
    z <= '1';  
  WHEN D =>  
    z <= w;  
END CASE;
```




Book sections covered

Chapter 2: Logic/VHDL (2.10 – 2.12)

Chapter 4: Combinational circuits (4.4 – 4.5)

Chapter 7: Sequential components (7.1 – 7.16)

Chapter 8: Sequential circuit design (8.1 – 8.4,
8.7 – 8.9)

Appendix A: VHDL reference



THANKS