



# **COL215 DIGITAL LOGIC AND SYSTEM DESIGN**

Divider Design  
13 September 2017

# Division: example

0100 | 00001101    ← Q  
          0011    ← A

↑  
B

0000000    ←  $0 \times B \times 2^3$   
00001101

0000000    ←  $0 \times B \times 2^2$   
00001101

01000    ←  $1 \times B \times 2^1$   
00000101

0100    ←  $1 \times B \times 2^0$   
00000001    ← R

# Unsigned Division

$$A = Q \times B + R$$

```
R = A; Q = 0; D = B
for i in 0 to n - 1 loop
  if (D x 2n-i-1 ≤ R) then
    R = R - D x 2n-i-1
    Qn-i-1 = 1
  else Qn-i-1 = 0
  end if
end loop
```

# Unsigned Division

$$A = Q \times B + R$$

```
R = A; Q = 0; D = B
for i in 0 to n - 1 loop
  if (D × 2n-i-1 ≤ R) then
    R = R - D × 2n-i-1
    Qn-i-1 = 1
  else Qn-i-1 = 0
  end if
end loop
```

can this be avoided ?

# Introducing shift registers

$$A = Q \times B + R$$

$R = A; Q = 0; D = B \times 2^{n-1}$

for  $i$  in 0 to  $n - 1$  loop

if  $(D \leq R)$  then

$R = R - D$

$Q = 2 \times Q + 1$


else  $Q = 2 \times Q$

end if

$D = D / 2$

end loop

# Divider design - 1

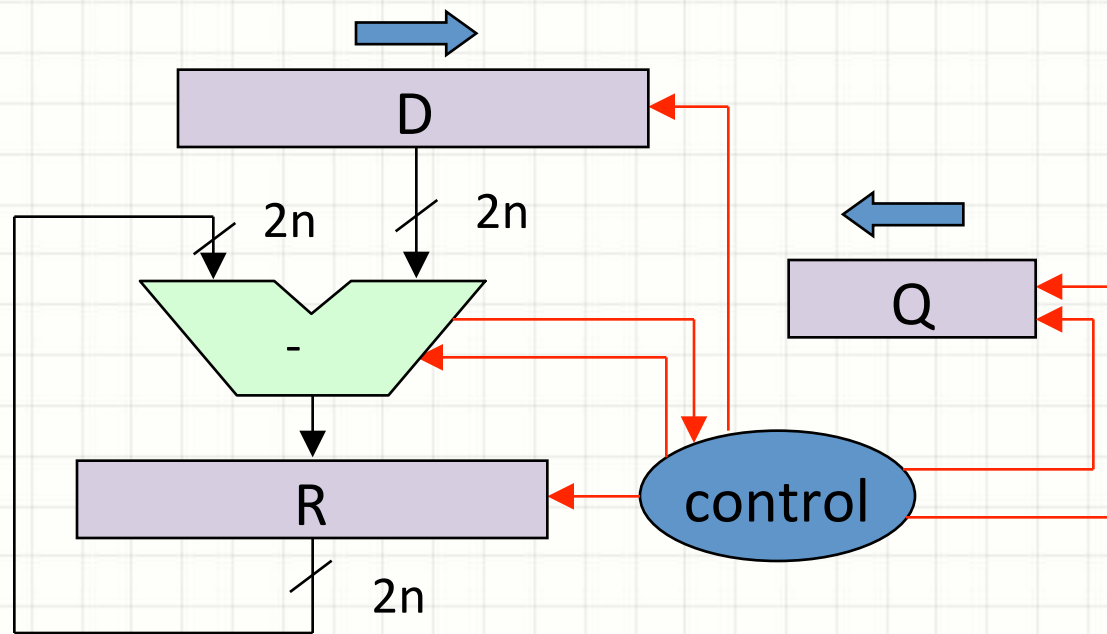

# Reducing subtractor size

$$A = Q \times B + R$$

$R = A; Q = 0; D = B$

for  $i$  in 0 to  $n - 1$  loop

$R = 2 \times R$

if  $(D \leq R_H)$  then

$R_H = R_H - D$

$Q = 2 \times Q + 1$

else  $Q = 2 \times Q$

end if

end loop

# Division: example


0100 | 00001101 ← Q  
          00011010 ← A  
          0000  
          00011010  
          00110100  
          0000  
          00110100  
          01101000  
          0100  
          00101000  
          01010000  
          0100  
          00010000 ← R

↑  
B

← 0 x B  
← 0 x B  
← 1 x B  
← 1 x B



# Divider design - 2

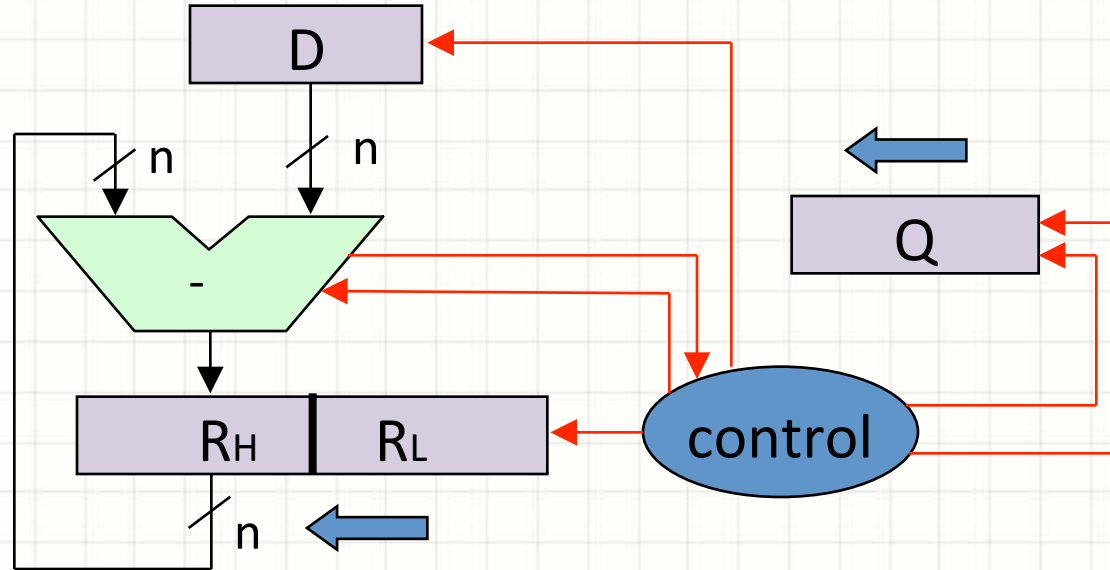

# Reducing registers

$$A = Q \times B + R$$

$R = A; D = B$

for  $i$  in 0 to  $n - 1$  loop

$R = 2 \times R$

if  $(D \leq R_H)$  then

$R_H = R_H - D$


$R = R + 1$

end if

end loop

#  $R_H$  = remainder,  $R_L$  = quotient

# Divider design - 3

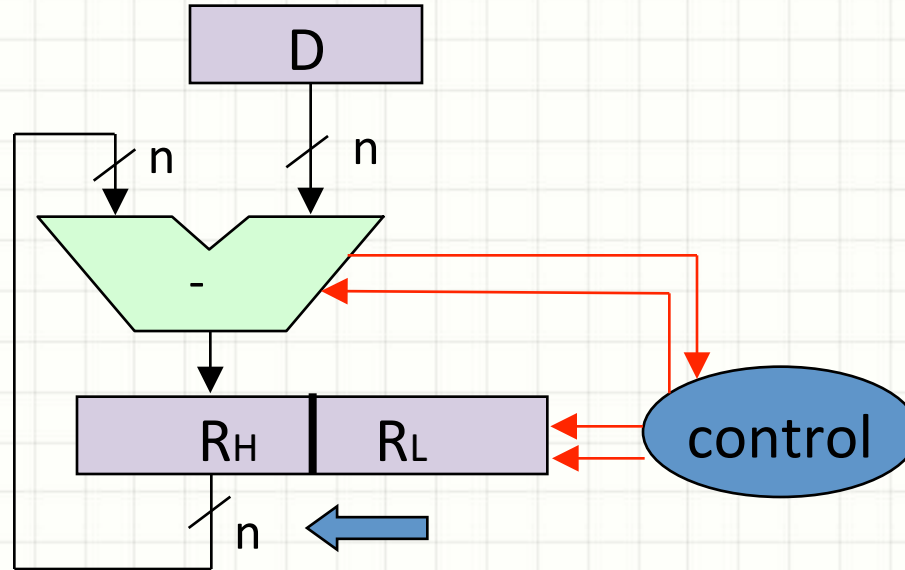

# Restoring division

- Non-restoring division
  - First compare the remaining dividend with divisor
  - Subtract only if dividend is large enough
- Restoring division
  - Subtract without comparing
  - Add (restore) the divisor if subtraction result negative

# Signed multiplication/division

- Handle sign and magnitude separately
- Directly multiply/divide signed integers

Dividend	Divisor	Quotient	Remainder
+	+	+	+
-	+	-	-
+	-	-	+
-	-	+	-

# Direct signed multiplication

- Use a common expression representing the values of positive as well as negative integers

$$B = -B_{n-1} \cdot 2^{n-1} + \sum_{i=0}^{n-2} B_i \cdot 2^i$$

# Common expr for +/- integers

$$\text{for } B \geq 0, B = \sum_{i=0}^{n-1} B_i \cdot 2^i = -B_{n-1} \cdot 2^{n-1} + \sum_{i=0}^{n-2} B_i \cdot 2^i \quad (\because B_{n-1} = 0)$$

$$\text{for } B < 0, B = -|B|$$

$$\text{now } |B| = 2^n - \sum_{i=0}^{n-1} B_i \cdot 2^i$$

$$\therefore B = -2^n + B_{n-1} \cdot 2^{n-1} + \sum_{i=0}^{n-2} B_i \cdot 2^i$$

$$= -B_{n-1} \cdot 2^{n-1} + \sum_{i=0}^{n-2} B_i \cdot 2^i \quad (\because B_{n-1} = 1)$$

# Direct signed multiplication

$$\begin{aligned} B &= -B_{n-1} \cdot 2^{n-1} + \sum_{i=0}^{n-2} B_i \cdot 2^i \\ &= -B_{n-1} \cdot 2^{n-1} + B_{n-2} \cdot 2^{n-2} + \dots + B_0 \cdot 2^0 \\ &= -B_{n-1} \cdot 2^{n-1} + 2B_{n-2} \cdot 2^{n-2} - B_{n-2} \cdot 2^{n-2} + \dots + 2B_0 \cdot 2^0 - B_0 \cdot 2^0 \\ &= -B_{n-1} \cdot 2^{n-1} + B_{n-2} \cdot 2^{n-1} - B_{n-2} \cdot 2^{n-2} + \dots + B_0 \cdot 2^1 - B_0 \cdot 2^0 \\ &= \sum_{i=0}^{n-1} (B_{i-1} - B_i) \cdot 2^i \quad \text{where } B_{-1} = 0 \end{aligned}$$

$$\therefore A \cdot B = \sum_{i=0}^{n-1} A \cdot (B_{i-1} - B_i) \cdot 2^i$$

Booth's algorithm



# Comparing with unsigned case

## unsigned multiplication

$B_i$       operation

0      no addition

1      add A

## signed multiplication

$B_i, B_{i-1}$       operation

0 0      no addition

0 1      add A

1 0      subtract A

1 1      no addition

# Original motivation for Booth's algorithm

Reduce the number of additions required

..... 0 0 0 1 1 1 1 1 1 0 0 0 .....

└──┘

↑

add

└──┘

↑

subtract

+ 1 0 0 0 0 0 0 0

- 0 0 0 0 0 0 0 1

---

0 1 1 1 1 1 1

# What have we learnt?

- Logic design (combinational circuits) [2, 4]
  - truth tables, expressions, circuits, VHDL
- Logic design (sequential circuits) [7, 8]
  - state transition tables, diagrams, circuits, VHDL
- Combinational & sequential modules [6, 7]
  - mux, demux, decoders, encoders, VHDL
  - flip-flops, registers, counters, VHDL
- From logic to arithmetic [5]
  - representations, conversions
  - operations and operators (add, subtract, compare, multiply, divide)

# What lies ahead?

- Technology [3]
  - transistor to FPGA and things in between
- A little more theory [4, 8, 9]
  - minimizing logic, minimizing states
- System design [10]
  - from algorithmic description to circuits
  - control-data partition
- Testing [11]
  - testing tools, design for testability



**THANKS**