

Left neighbour	Your Name	Your Entry No.	Right neighbour

**COL215 Digital Logic and System Design Quiz 4 16.11.2017**

**Q 1.** A VHDL description below uses a case statement in a process. Give an equivalent VHDL description for the architecture without using any of the following - process, case statement, if statement, conditional signal assignment and selected signal assignment.

<pre> entity example is     port (         s : input bit_vector (1 downto 0);         y : output bit_vector (3 downto 0)     ) </pre>	
<pre> architecture casestmt of example is begin     process (s)     begin         case s is             when "00"    =&gt; y &lt;= "0001";             when "01"    =&gt; y &lt;= "0010";             when "10"    =&gt; y &lt;= "0100";             when others   =&gt; y &lt;= "1000";         end case;     end process; end architecture casestmt; </pre>	<pre> architecture dataflow of example is begin     y (0) &lt;= not s (1) and not s (0);     y (1) &lt;= not s (1) and s (0);     y (2) &lt;= s (1) and not s (0);     y (3) &lt;= s (1) and s (0); end architecture dataflow; </pre> <p align="right"><b>[1 mark]</b></p> <p>Another way:</p> <pre> architecture dataflow of example is begin     y &lt;= (not s (1) and not s (0)) &amp;         (not s (1) and s (0)) &amp;         (s (1) and not s (0)) &amp;         (s (1) and s (0)); end architecture dataflow; </pre>

Left neighbour	Your Name	Your Entry No.	Right neighbour

**COL215 Digital Logic and System Design Quiz 4 16.11.2017**

**Q 2.** Consider addition of two  $n$ -bit signed integers using 2's complement representation. Show that when two numbers with opposite signs are added, carries  $c_n$  and  $c_{n-1}$  are always equal. What does it imply about overflow?

**Solution:**

Let the two numbers be  $A = a_{n-1} a_{n-2} \dots a_1 a_0$  and  $B = b_{n-1} b_{n-2} \dots b_1 b_0$ .

Without any loss of generality, let us assume that  $A$  is non-negative and  $B$  is negative. That is,  $a_{n-1} = 0$  and  $b_{n-1} = 1$ . Let us now examine addition of  $a_{n-1}$  and  $b_{n-1}$  with carry  $c_{n-1}$ .

Case (i)

Let  $c_{n-1} = 0$

Addition of  $a_{n-1}$  and  $b_{n-1}$  with carry  $c_{n-1}$  means adding 0, 1 and 0.

We get carry  $c_n = 0$ , which is same as  $c_{n-1}$

Case (ii)

Let  $c_{n-1} = 1$

Addition of  $a_{n-1}$  and  $b_{n-1}$  with carry  $c_{n-1}$  means adding 0, 1 and 1.

We get carry  $c_n = 1$ , which is again same as  $c_{n-1}$

This shows that in both cases  $c_n = c_{n-1}$ .

[1/2 mark]


This condition implies absence of overflow, which is consistent with the fact that the magnitude of the sum of two oppositely signed numbers will always be less than or equal to the magnitude of each of the numbers.

[1/2 mark]


Left neighbour	Your Name	Your Entry No.	Right neighbour

**COL215 Digital Logic and System Design Quiz 4 16.11.2017**

 **Q 3.** In the circuit shown below, the input C is a square wave with time period = 8 units. Draw the waveforms for signals x, y1 and y2, assuming the delay of each gate (NOR as well as NOT) to be 1 unit.



 
1 mark if all 3 waveforms are correct.  
 ½ mark if 2 waveforms are correct.



Left neighbour	Your Name	Your Entry No.	Right neighbour

**COL215 Digital Logic and System Design Quiz 4 16.11.2017**

 **Q 4.** Test input generation for e stuck\_at\_0 fault is being attempted for the circuit shown below using D - algorithm. Which input combination will result in cancellation of D and  $\bar{D}$ ? What will be observed at output f under that condition?



$\bar{D}$  at the fault site results in D at the output of the inverter. These propagate through the OR gates if these gates have other inputs 0. Then these get cancelled at the AND gate. Input combination which cause this is  $w1, w2, w3, w4, w5 = 0x110$  or  $w1, w2, w3, w4, w5 = x0110$ . (D and  $\bar{D}$  are interchangeable).

[1 mark for any of the two answers]