



# COL215 DIGITAL LOGIC AND SYSTEM DESIGN

## VHDL

- switch example
- sequential circuits

22 August 2017

# 3-Port Switch


ENTITY Switch3 IS

PORT (


req : IN bit\_vector (2 downto 0);  
ack : OUT bit\_vector (2 downto 0);  
din : IN bit\_vector (2 downto 0);  
dout : OUT bit\_vector (2 downto 0);  
dest2 : IN bit\_vector (1 downto 0);  
dest1 : IN bit\_vector (1 downto 0);  
dest0 : IN bit\_vector (1 downto 0);  
src : OUT bit\_vector (1 downto 0)

);

END Switch3;

 

# 3-Port Switch Design

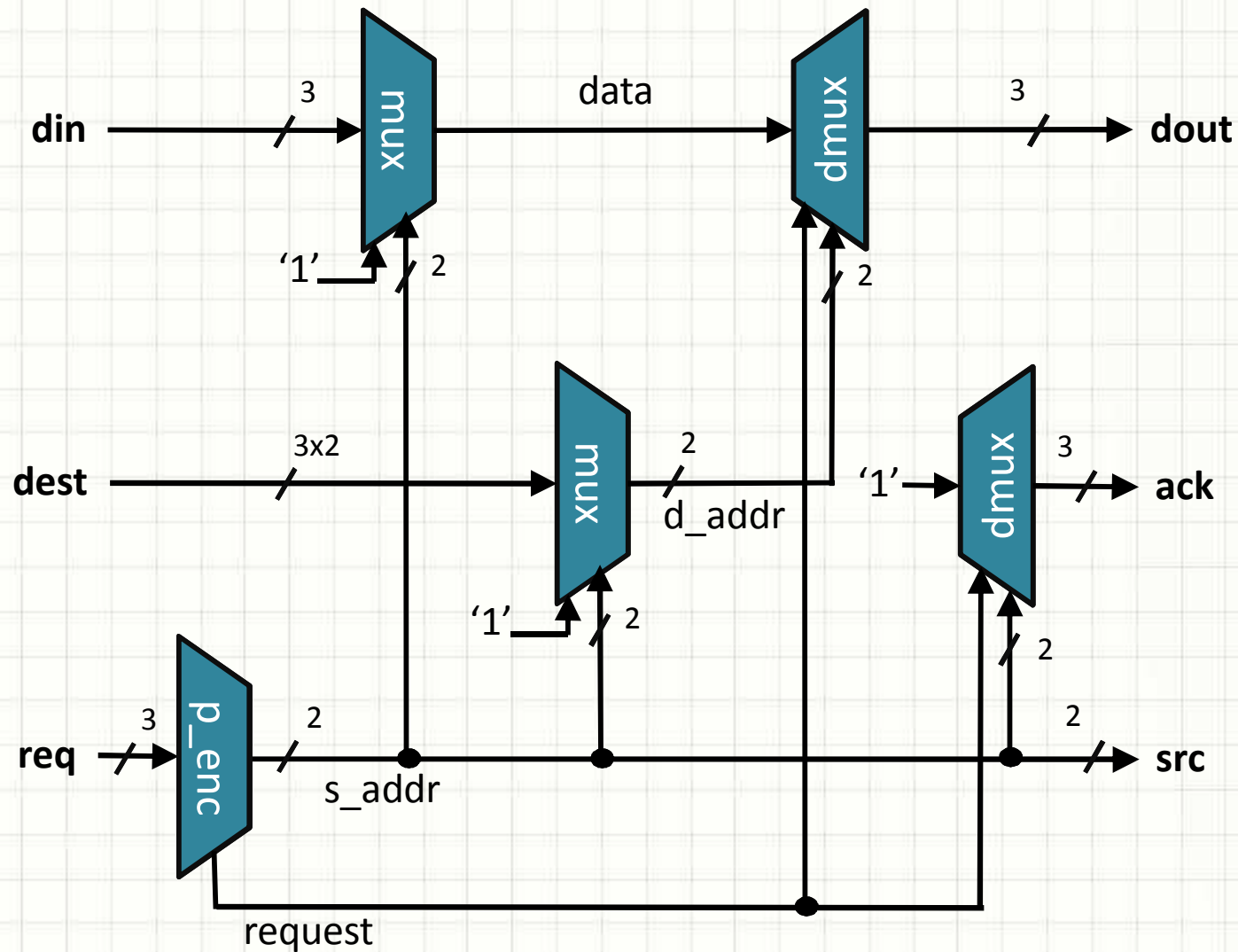

# VHDL statements learned so far

## Concurrent

- Concurrent signal assignment
- Selected signal assignment
- Conditional signal assignment
- Process statement
- Component instantiation statement

## Sequential

- [Sequential] signal assignment
- Case statement
- If statement

← To be introduced today

```

ENTITY mux_3_1 IS
  PORT (X: IN bit_vector (2 downto 0);
        S: IN bit_vector (1 downto 0);
        e: IN bit;
        y: OUT bit
  );

```

```

END mux_3_1;

```

```



ENTITY mux_3_1_2bit IS
  PORT (X2: IN bit_vector (1 downto 0);
        X1: IN bit_vector (1 downto 0);
        X0: IN bit_vector (1 downto 0);
        S: IN bit_vector (1 downto 0);
        e: IN bit;
        y: OUT bit_vector (1 downto 0)
  );

```

```

END mux_3_1_2bit;

```

  

```
ENTITY de-mux_1_3 IS
```

```
  PORT (x: IN  bit;
```

```
        e: IN  bit;
```

```
        S: IN  bit_vector (1 downto 0);
```

```
        Y: OUT bit_vector (2 downto 0)
```

```
  );
```

```
END de-mux_1_3;
```

```
ENTITY Priority_3 IS
```



```
  PORT (X: IN  bit_vector (2 downto 0);
```

```
        S: OUT bit_vector (1 downto 0);
```

```
        e: OUT bit
```

```
  );
```

```
END Priority_3;
```

  



# 3-Port Switch

ARCHITECTURE structural OF Switch3 IS

BEGIN

SIGNAL s\_addr, d\_addr : bit\_vector (1 downto 0);


SIGNAL request, data : bit;

SIGNAL one :bit := '1'

src <= s\_addr;

{component instantiations}


END ARCHITECTURE structural;

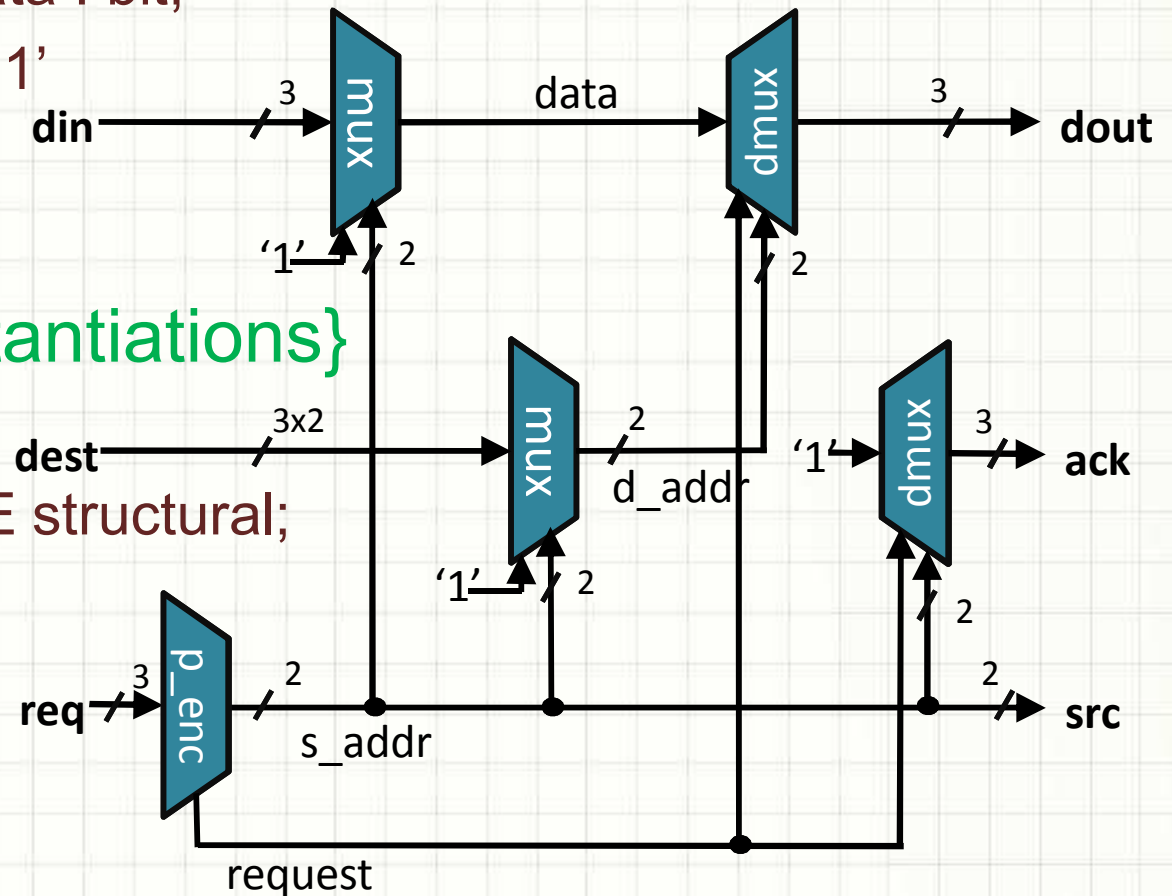
 
# Component instantiations

Priority\_encoder:


```
ENTITY WORK.Priority_3 (cond)  
  PORT MAP (req, s_addr, request);  
  positional association
```



definition

Priority\_encoder:
 
```
ENTITY WORK.Priority_3 (cond)  
  PORT MAP (  
    x => req,      named association  
    s => s_addr,  
    e => request  
  );
```



instance



# Component instantiations

Priority\_encoder: ENTITY WORK.Priority\_3 (cond)  
PORT MAP (req, s\_addr, request);

Data\_mux: ENTITY WORK.mux\_3\_1 (ssa)  
PORT MAP (din, s\_addr, one, data);

Addr\_mux: ENTITY WORK.mux\_3\_1\_2bit (ssa)  
PORT MAP (dest2, dest1, dest0, s\_addr, d\_addr);

Data\_dmux: ENTITY WORK.de-mux\_1\_3 (ssa)  
PORT MAP (data, request, d\_addr, dout);

Ack\_dmux: ENTITY WORK.de-mux\_1\_3 (ssa)  
PORT MAP (one, request, s\_addr, ack);

# 3-Port Switch

ARCHITECTURE combined OF Switch3 IS

BEGIN

SIGNAL s\_addr, d\_addr : bit\_vector (1 downto 0);

SIGNAL request, data : bit;

Priority\_encoder\_process;

Data\_mux\_process;

Addr\_mux\_process;

Data\_dmux\_process;

Ack\_dmux\_process;

src <= s\_addr;


END ARCHITECTURE combined;



# SEQUENTIAL CIRCUITS
 
# VHDL description of D Latch


```
ENTITY latch IS  
  PORT (D, C: IN BIT; Q, Q_ : OUT BIT);  
END latch;
```



```
ARCHITECTURE asynch OF latch IS  
  SIGNAL S_, R_      : BIT;  
BEGIN
```


```
  S_ <= C NAND D;  
  R_ <= C NAND (NOT D);  
  Q  <= S_ NAND Q_ ;  
  Q_ <= R_ NAND Q  ;
```

```
END asynch;
```

 

 
# VHDL description of D Latch

```
ENTITY latch IS  
  PORT (D, C: IN BIT; Q, Q_ : OUT BIT);  
END latch;
```



```
ARCHITECTURE asynch OF latch IS  
  SIGNAL S_, R_, P, P_ : BIT;  
BEGIN
```
 
```
  S_ <= C NAND D;  
  R_ <= C NAND (NOT D);  
  P  <= S_ NAND P_ ;  
  P_ <= R_ NAND P  ;  
  Q  <= P;  
  Q_ <= P_ ;  
END asynch;
```




# Conditional signal assignment

ENTITY latch IS

PORT (D, C: IN BIT; Q, Q\_ : OUT BIT);  
END latch;

ARCHITECTURE csa OF latch IS

 SIGNAL P : BIT;  
BEGIN  
P <= D WHEN C = '1' ELSE P;  
Q <= P;  
Q\_ <= NOT P;  
END csa;






# Conditional signal assignment

ENTITY latch IS

PORT (D, C: IN BIT; Q, Q\_ : OUT BIT);  
END latch;

ARCHITECTURE csa OF latch IS

 
SIGNAL P : BIT;  
BEGIN  
P <= D WHEN C = '1' ELSE P;  
Q <= P;  
Q\_ <= NOT P;  
END csa;


 
# Two descriptions of D Latch

```
ENTITY latch IS
  PORT (D, C: IN BIT;
        Q, Q_ : OUT BIT);
END latch;
```


```
ARCHITECTURE asynch
  OF latch IS
    SIGNAL S_, R_, P, P_ : BIT;
  BEGIN
    S_ <= C NAND D;
    R_ <= C NAND (NOT D);
    P  <= S_ NAND P_;
    P_ <= R_ NAND P;
    Q  <= P;
    Q_ <= P_;
  END asynch;
```



```
ARCHITECTURE csa
  OF latch IS
    SIGNAL P : BIT;
  BEGIN
    P <= D WHEN C = '1';

    Q  <= P;
    Q_ <= NOT P;
  END csa;
```


# Master-Slave D Flip-Flop

 

ENTITY MSFF IS  
 PORT (D, C: IN BIT; Q : OUT BIT);  
 END MSFF;

ARCHITECTURE dual OF MSFF IS

 SIGNAL Qm : BIT;  
 BEGIN  
 Qm <= D WHEN C = '1';  
 Q <= Qm WHEN C = '0';  
 END dual;



# Clocked circuits

Check for  
'1' level

```
PROCESS (clk)
BEGIN
    IF clk = '1' THEN
        ..... first time on '1' level, later on rising edge
    END PROCESS;
```

Check for  
Rising edge

```
PROCESS (clk)
BEGIN
    IF clk = '1' AND clk'EVENT THEN
        ..... only on rising edge
    END PROCESS;
```

# D Flip-flop with Set/Reset

ENTITY DFFsr IS

PORT (d, clk, s, r: IN BIT;

q : OUT BIT);

END DFFsr;

# D Flip-flop with synch S/R

```
ARCHITECTURE synchronous OF DFFsr IS
BEGIN
  PROCESS (clk)
  BEGIN
    IF clk = '1' AND clk'EVENT THEN
      IF s = '1' THEN      q <= '1';
      ELSIF r = '1' THEN  q <= '0';
      ELSE                q <= d;
      END IF;
    END IF;
  END PROCESS;
END ARCHITECTURE synchronous;
```



# D Flip-flop with asynch S/R

ARCHITECTURE asynchronous OF DFFsr IS

BEGIN

PROCESS (clk, s, r)

BEGIN

IF s = '1' THEN q <= '1';

ELSIF r = '1' THEN q <= '0';

ELSIF clk = '1' AND clk'EVENT THEN q <= d;

END IF;

END PROCESS;

END ARCHITECTURE asynchronous;

# Multi-mode Register

ENTITY Reg8 IS

PORT (SLin, SRin, Clk : IN bit; SLout, SRout OUT bit;


A : IN bit\_vector (0 TO 7);

Mode : IN bit\_vector (1 downto 0);

Q : OUT bit\_vector (0 TO 7)

);

END ENTITY;

 

# Multi-mode Register

ARCHITECTURE beh OF Reg8 IS

SIGNAL t bit\_vector (0 TO 7) := "00000000";

BEGIN

PROCESS (Clk) BEGIN

IF (Clk = '1' AND clk'EVENT) THEN

CASE Mode IS

WHEN "00" => t <= t;

WHEN "01" => t <= SRin & t (0 TO 6);

WHEN "10" => t <= t (1 TO 7) & SLin;

WHEN "11" => t <= A;

END CASE;

END IF;

END PROCESS;

Q <= t;

SLout <= Q(0);

SRout <= Q(7);

END ARCHITECTURE beh;

# Counter

ENTITY counter4 IS

PORT (

reset, clk : IN bit\_logic;

count : OUT bit\_vector (3 downto 0)

);

END ENTITY;

# Counter

ARCHITECTURE procedural OF counter4 IS

SIGNAL t : bit\_vector (3 downto 0);

BEGIN

PROCESS (clk) BEGIN

IF (clk = '0' AND clk'EVENT) THEN

IF (reset = '1') THEN t <= "0000";

ELSE t <= t + 1;

END IF;

END IF;

END PROCESS;

count <= t;

END ARCHITECTURE procedural;



**THANKS**